



## Lecture 5

# Computer Architecture

Slide deck for Chapter 5 of the book


*The Elements of Computing Systems* (2<sup>nd</sup> edition)

By Noam Nisan and Shimon Schocken


MIT Press

# Nand to Tetris Roadmap: Hardware


---

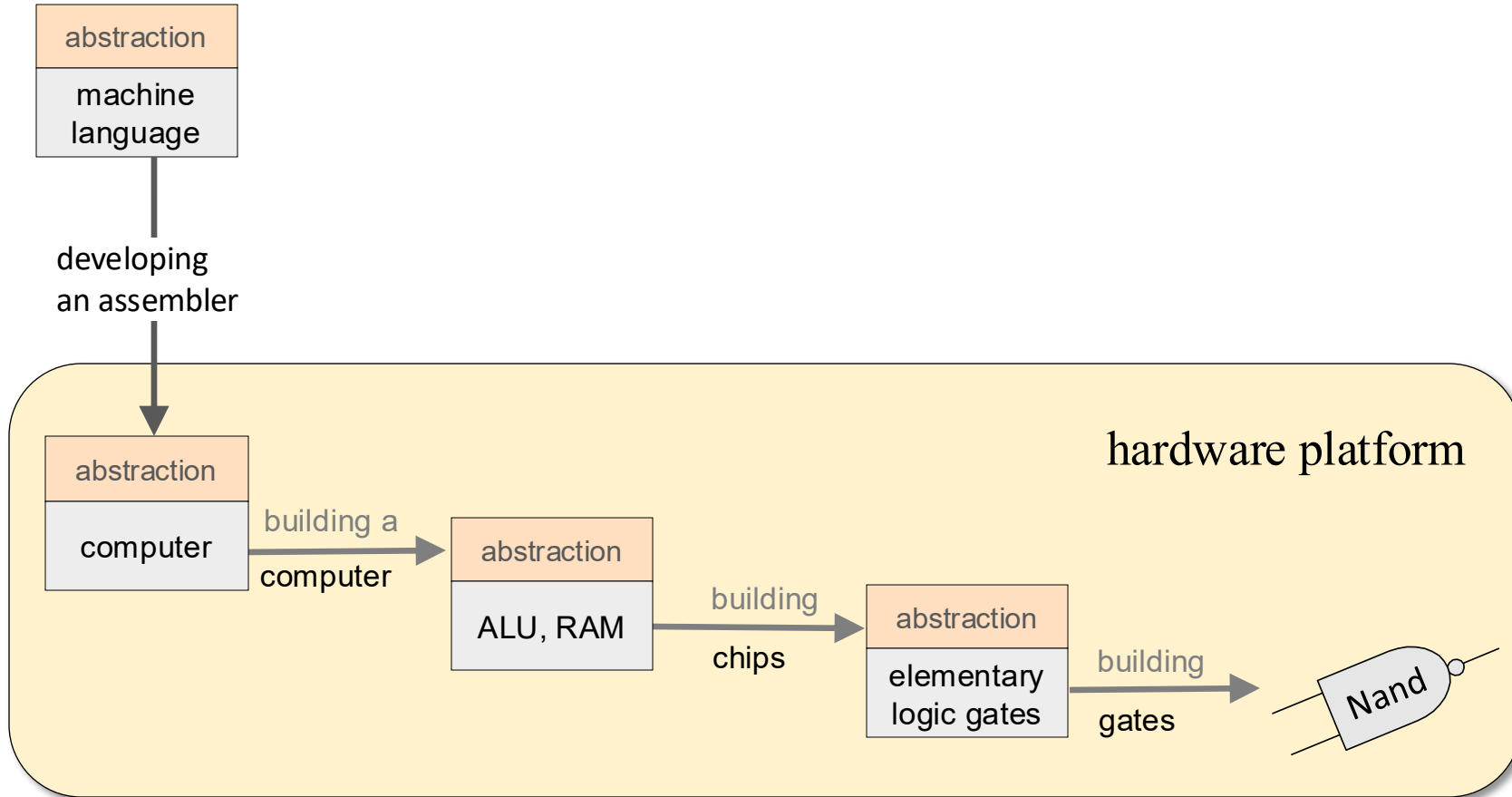

# Nand to Tetris Roadmap: Hardware

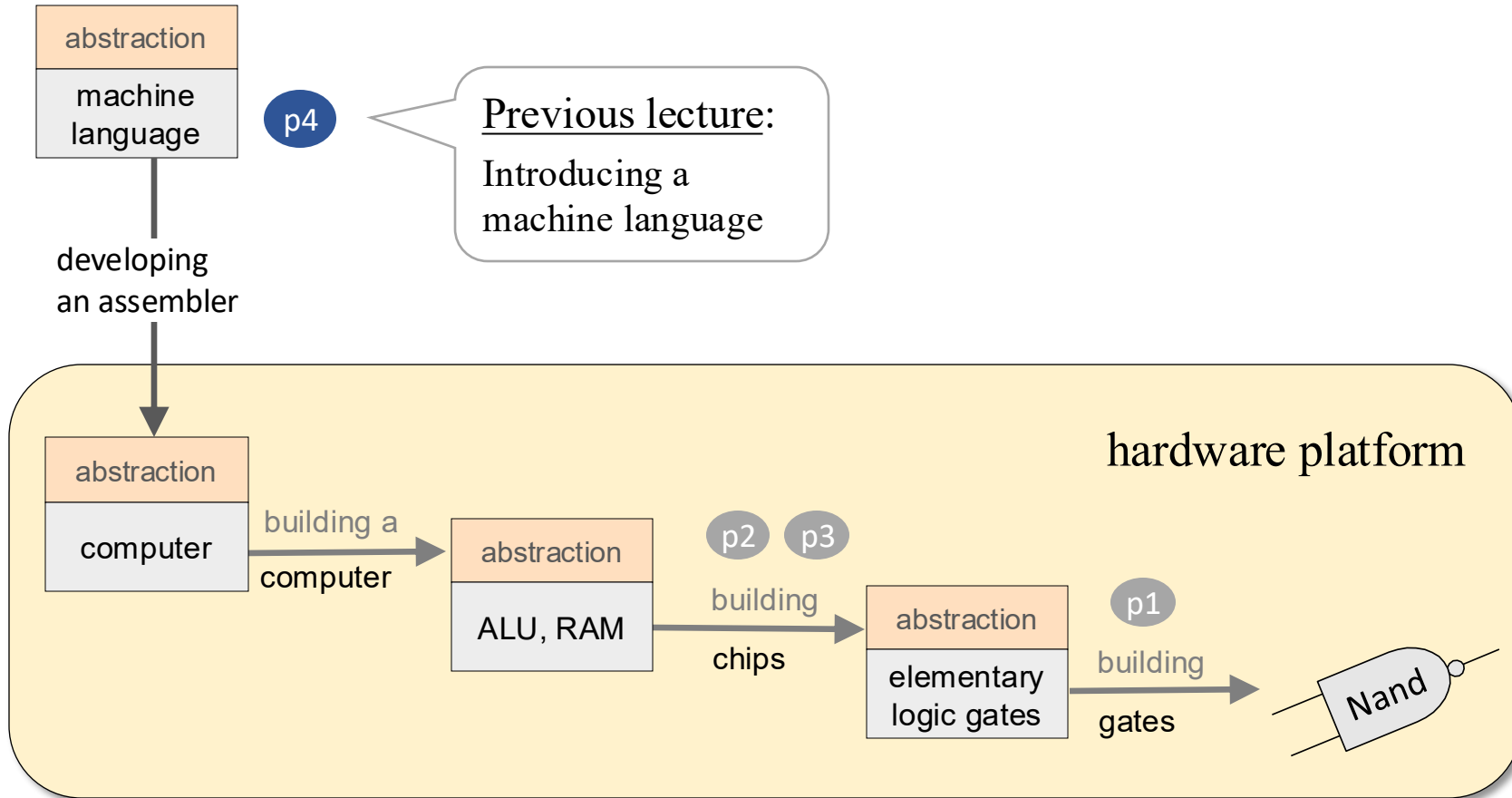

# Nand to Tetris Roadmap: Hardware

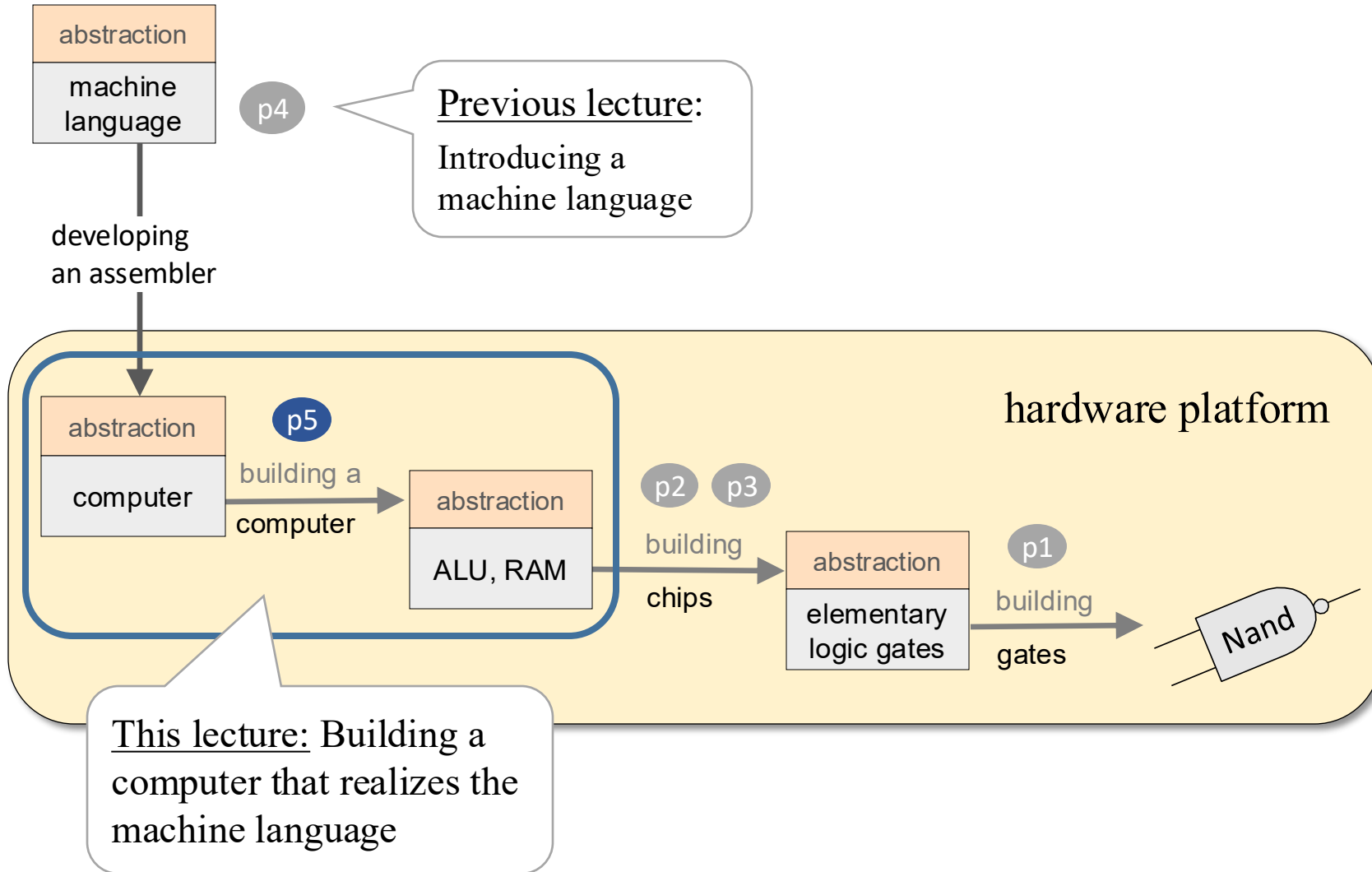


# Nand to Tetris Roadmap: Hardware
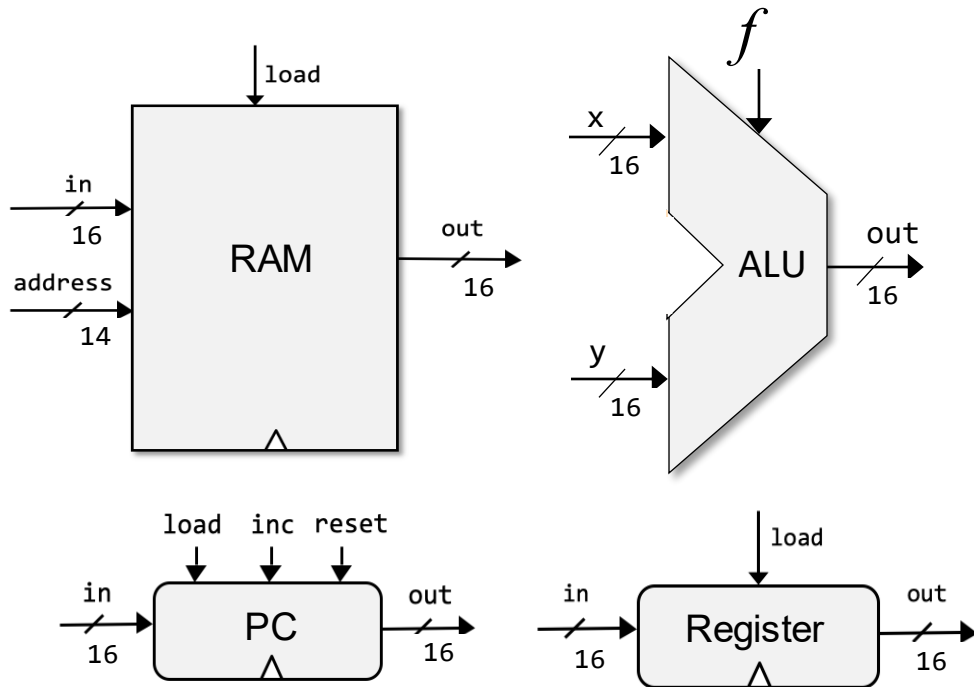
## The challenge

Integrate the chips built  
in chapters 1, 2, 3...


... into an architecture that  
executes *any program* written in  
the machine language introduced  
in chapter 4



```
// Computes R1 = 1 + 2 + 3 + ... + R0
// i = 1
@i
M=1
// sum = 0
@sum
M=0
(LOOP)
// if(i > R0) goto STOP
@i
D=M
@R0
D=D-M
@STOP
D;JGT
...
```

# Computer Architecture

---

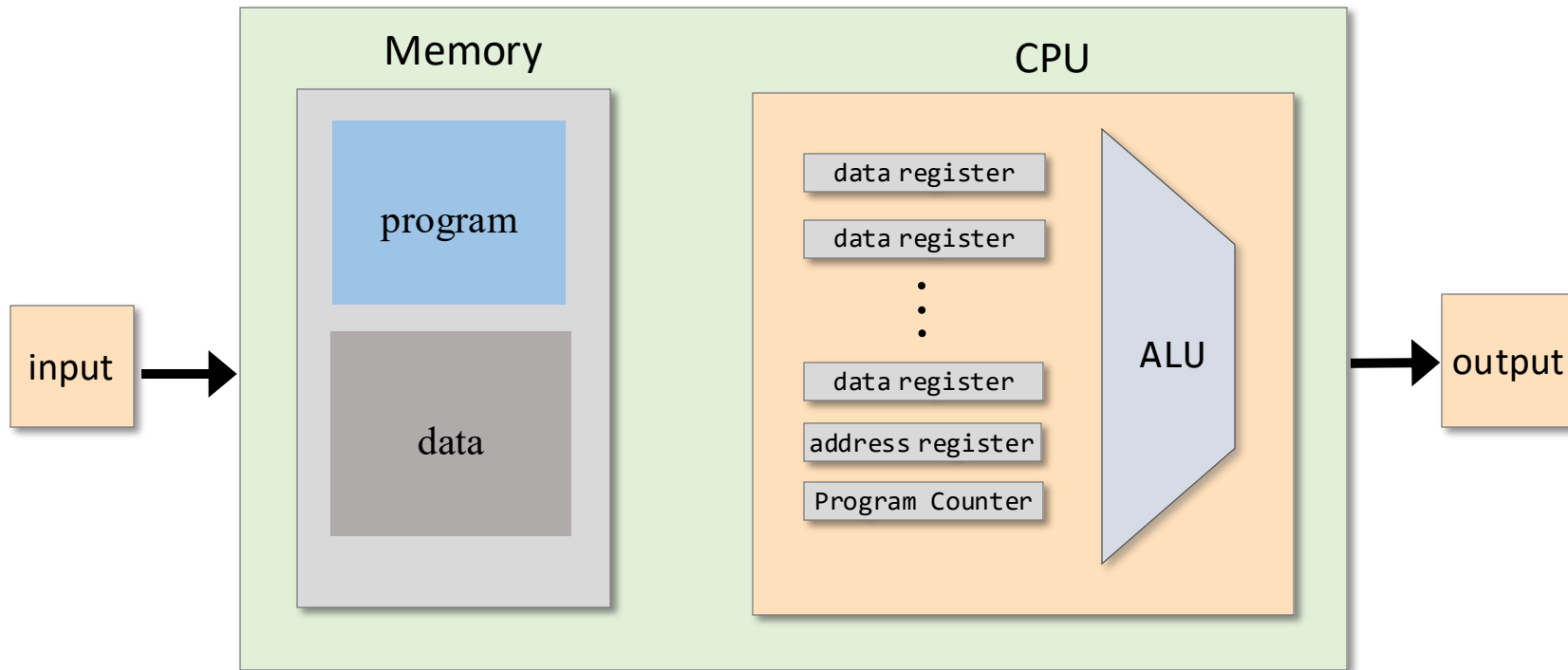

- Processor, registers, memory
- Stored program concept
- *General-purpose*

We'll build the Hack computer – a variant of this architecture.

# Computer Architecture

---



## Basic architecture

- Fetch-Execute cycle
- The Hack CPU
- Input / output
- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines

# Early computers: 17<sup>th</sup> century




Blaise Pascal  
1623 – 1662




## Pascal's Calculator (*Pascaline*, 1652)

- Add
- Subtract

 



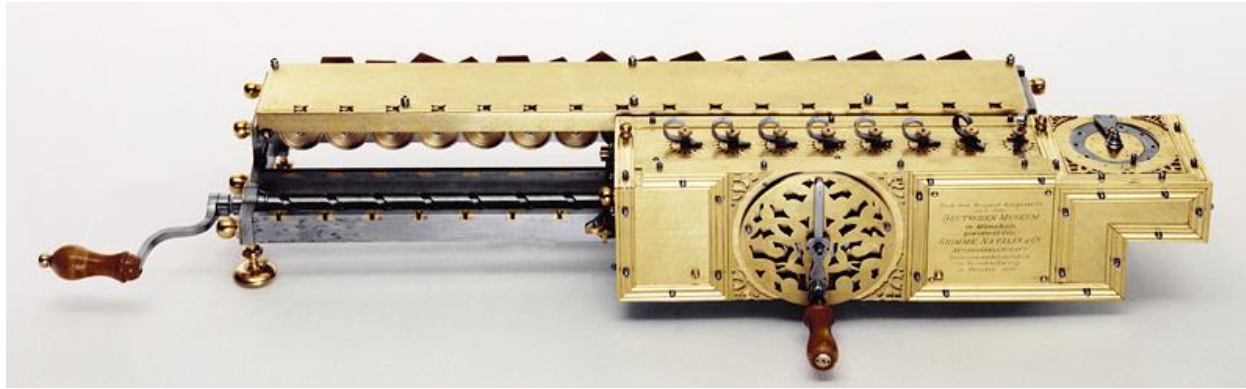
# Early computers: 17<sup>th</sup> century




Gottfried Leibniz  
1646 – 1716

## Leibniz Calculator (1673)

- Add
- Subtract
- Multiply
- Divide.

 

 
# Early computers: 17<sup>th</sup> century



Gottfried Leibniz  
1646 – 1716

## Leibniz Calculator (1673)


- Add
- Subtract
- Multiply
- Divide.

 


Side benefits:  
Advances in  
gears /  
mechanical  
engineering

# Early computers: 19<sup>th</sup> century

---

 

mechanical loom  
(Jacquard, 1804)

 

mechanical calculator  
(Babbage, 1837)

Milestone:  
punched cards / software  
**Programmable!**



# Modern computers: 20<sup>th</sup> century

---



John Von Neumann



John Mauchly



Presper Eckert




John Atanasoff



Howard Aiken




Konrad Zuse

 

ENIAC: First digital, programmable,  
stored program computer

University of Pennsylvania, 1946,

 (Inspired by many other  
early computers and innovators)



Colossus: First digital, programmable,  
computer, UK, 1945




Tommy Flowers
 
# Modern computers: 20<sup>th</sup> century

---



Kathleen McNulty, Jean Jennings, Frances Snyder,  
Marlyn Wescoff, Frances Bilas, Ruth Lichterman



## Eniac women

Pioneered reusable code, subroutines,  
flowcharts, compilation, ...  
many other software innovations



Grace Hopper



Adele Koss

Compilation pioneers

# Modern computers: 20<sup>th</sup> century

---

Same **hardware** can run many different programs (**software**)




“If it should turn out that the basic logic of a machine designed for the numerical solution of differential equations coincides with the logic of a machine intended to make bills for department stores, I would regard this as the most amazing coincidence I have ever encountered” — Howard Aiken (Mark 1 computer architect, 1956)

“The *stored program computer*, as conceived by Alan Turing and delivered by John von Neumann, broke the distinction between numbers that *mean things* and numbers that *do things*. Our universe would never be the same” ([George Dyson](#))

# Basic architecture

---

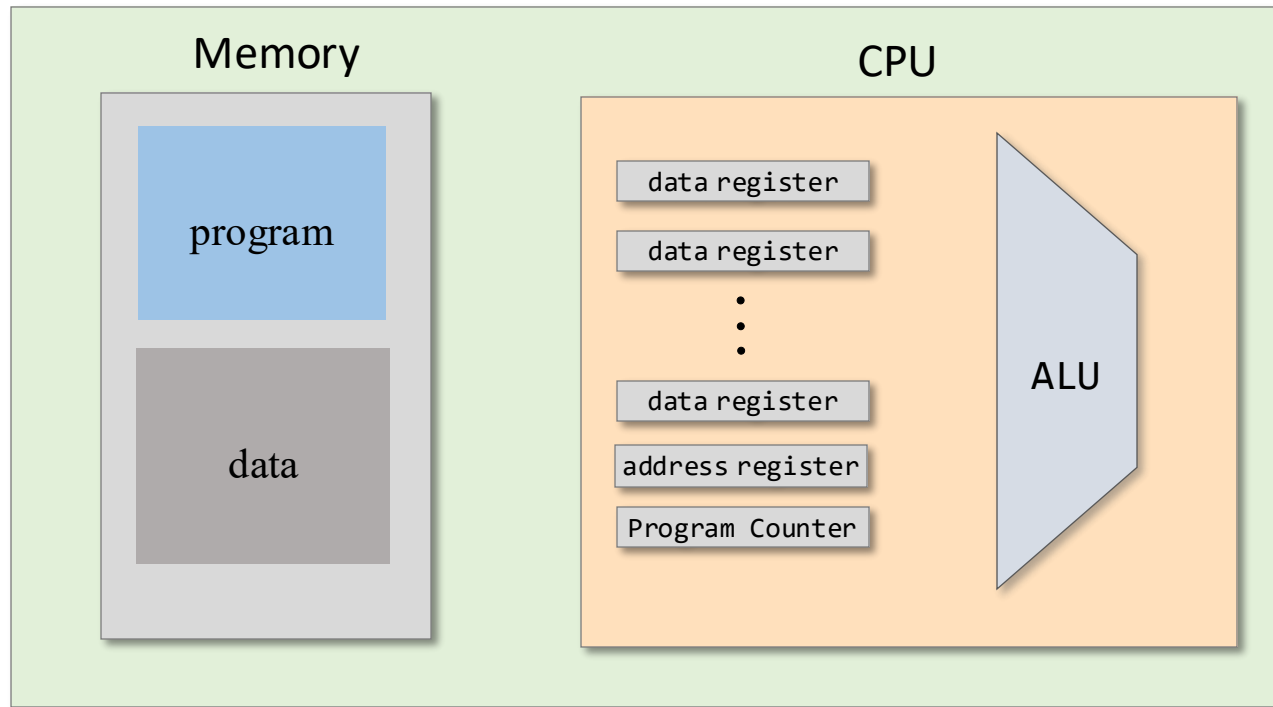


Computer:

A machine that uses instructions to manipulates data


# Basic architecture

---

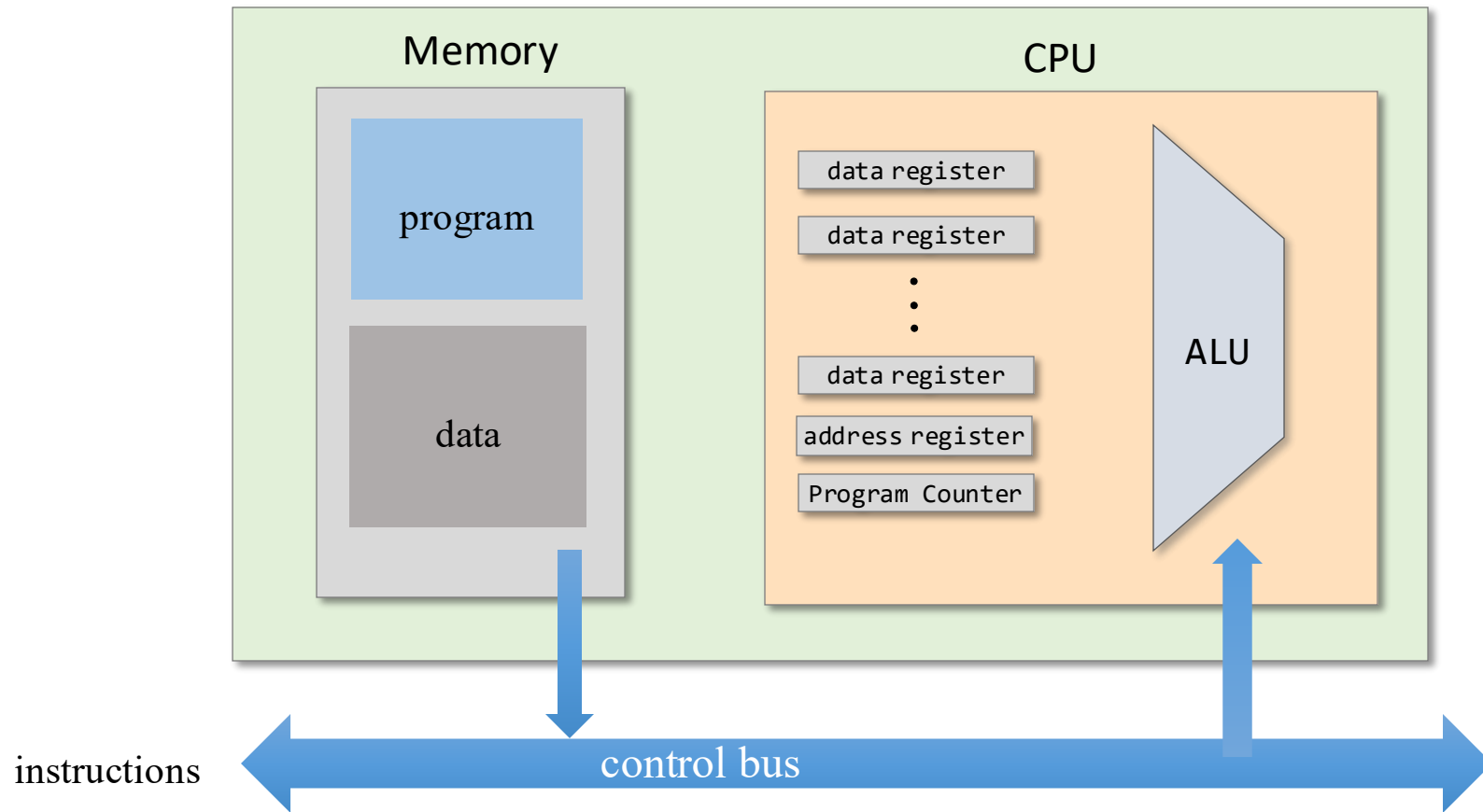




# Basic architecture

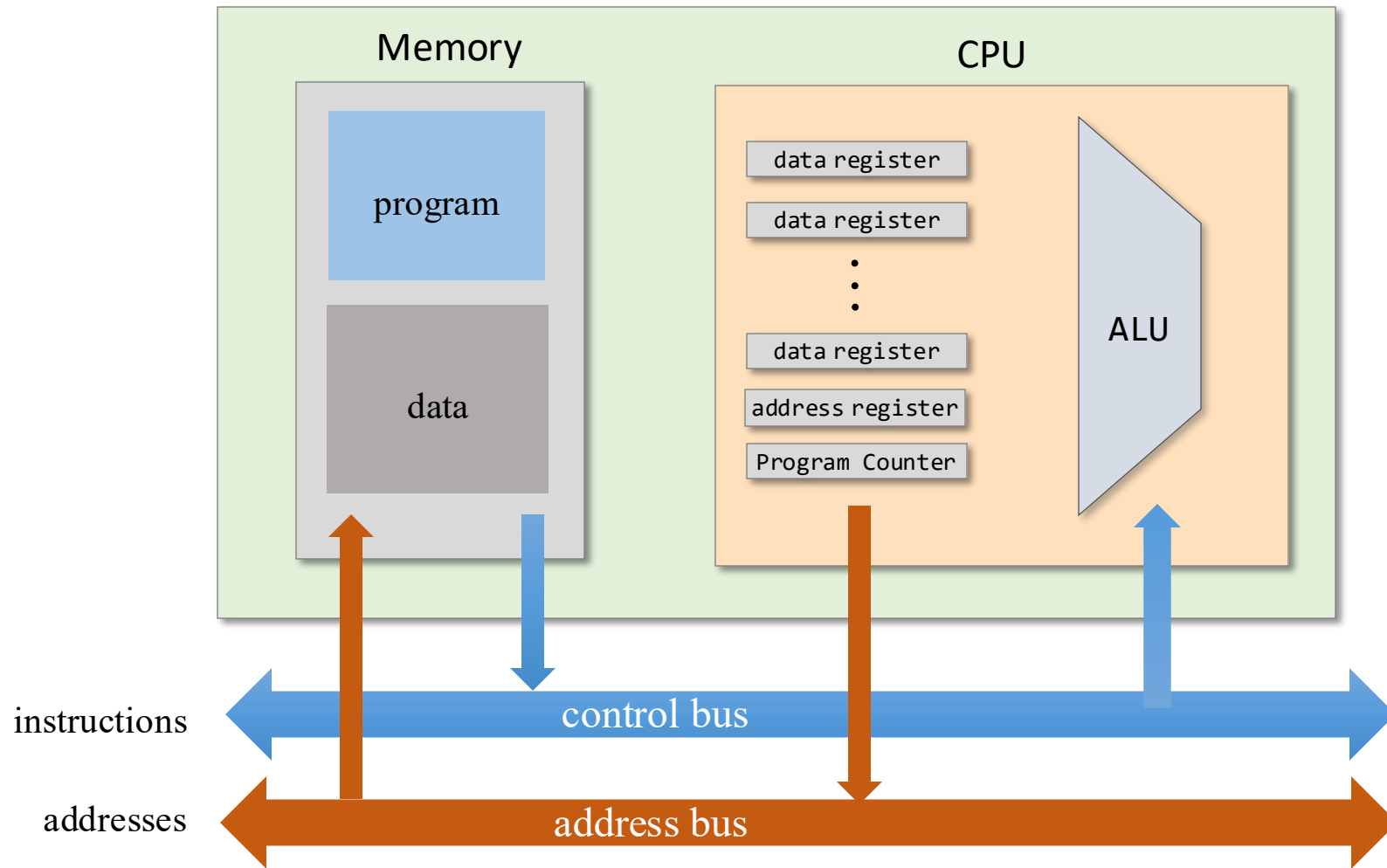

# Basic architecture

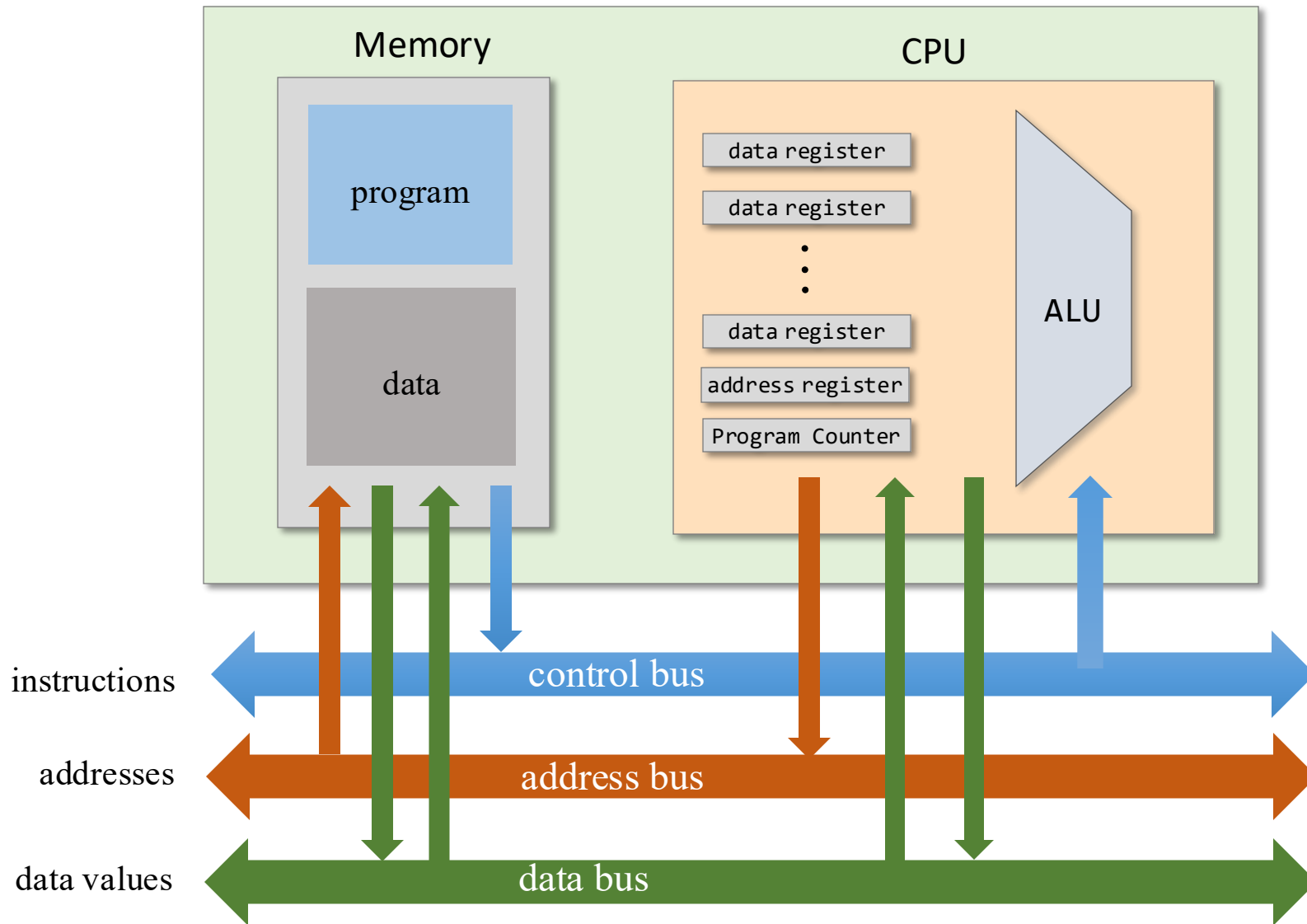

The computer can be viewed as a set of chips, connected by pathways (buses).

# Computer architecture

---


✓ Basic architecture

➡ Fetch-Execute cycle

- The Hack CPU
- Input / output
- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines

# Computer architecture


---

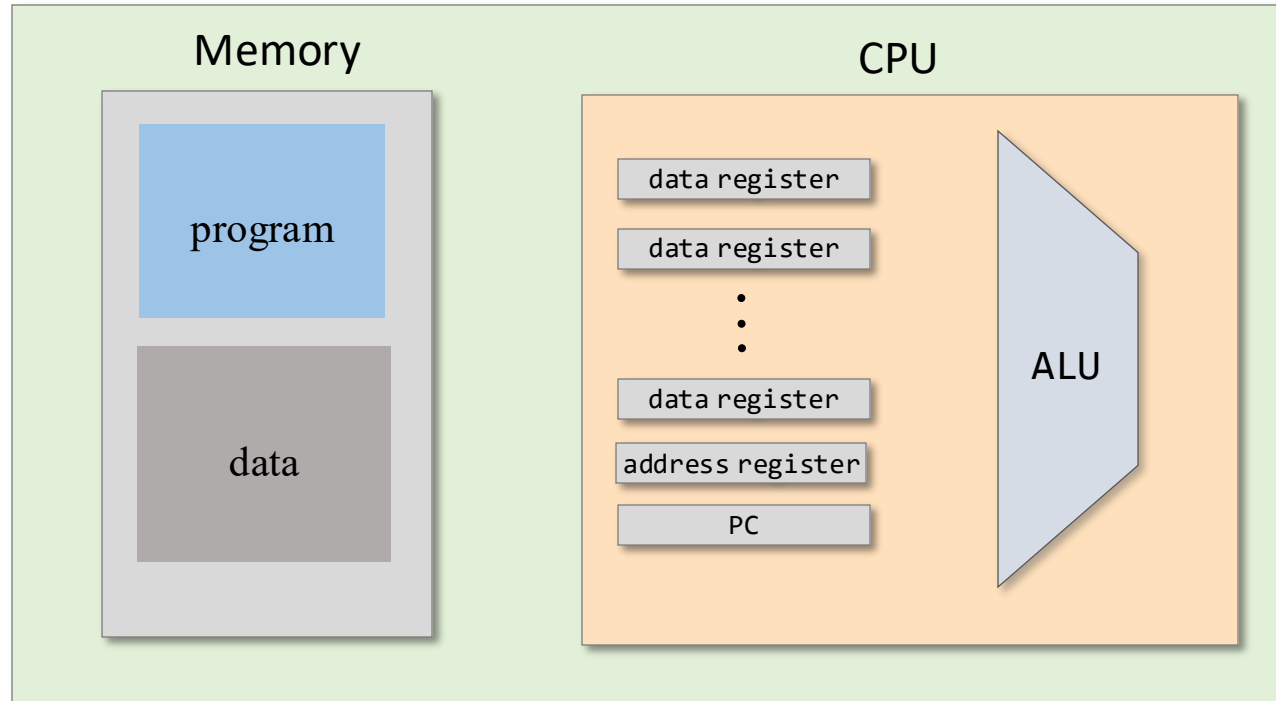


## Basic loop

- ***Fetch***  
an instruction  
(by supplying  
an address)
- ***Execute***  
the instruction  
(and figure out the  
address of the next  
instruction)


# Computer architecture

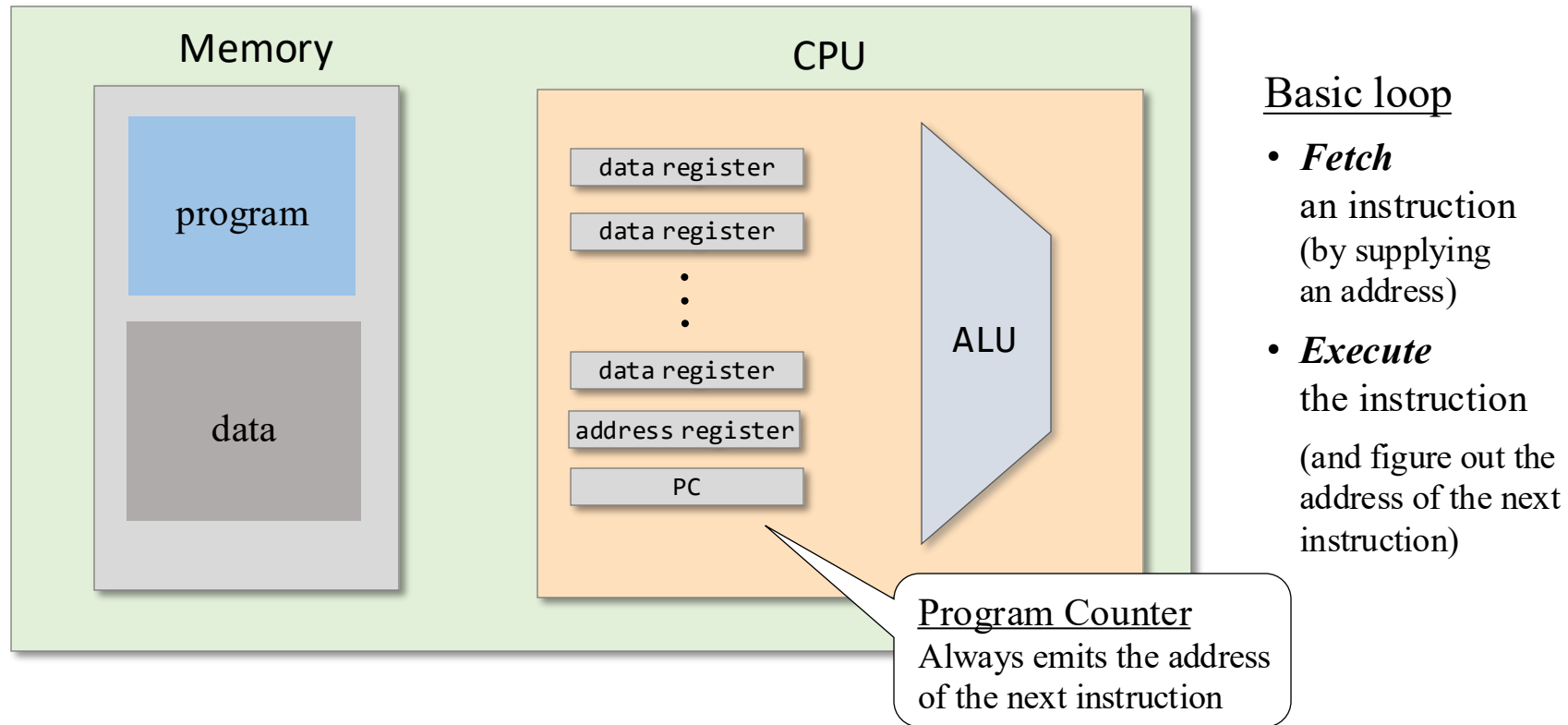


# Fetch an instruction

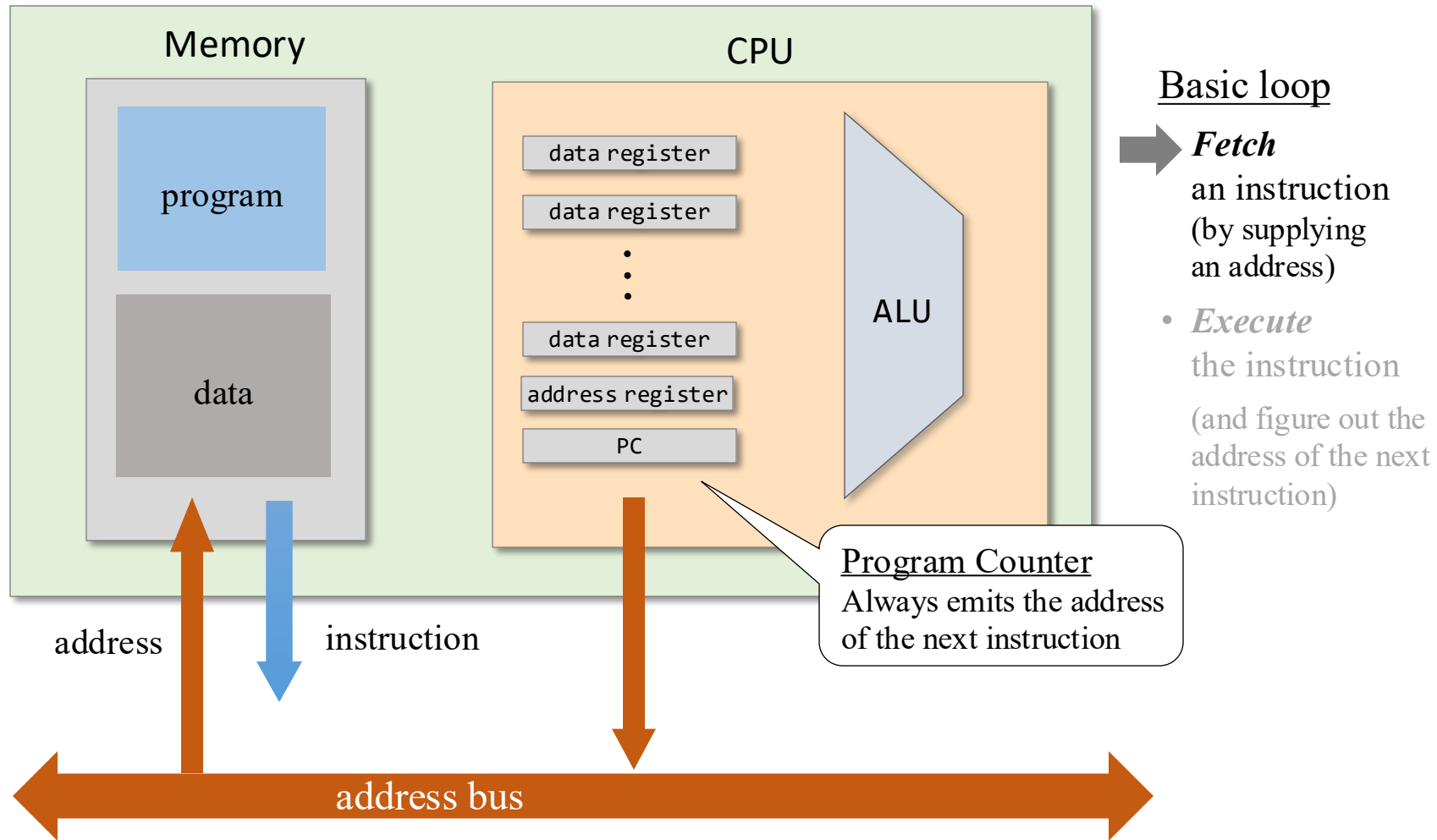

# Fetch an instruction

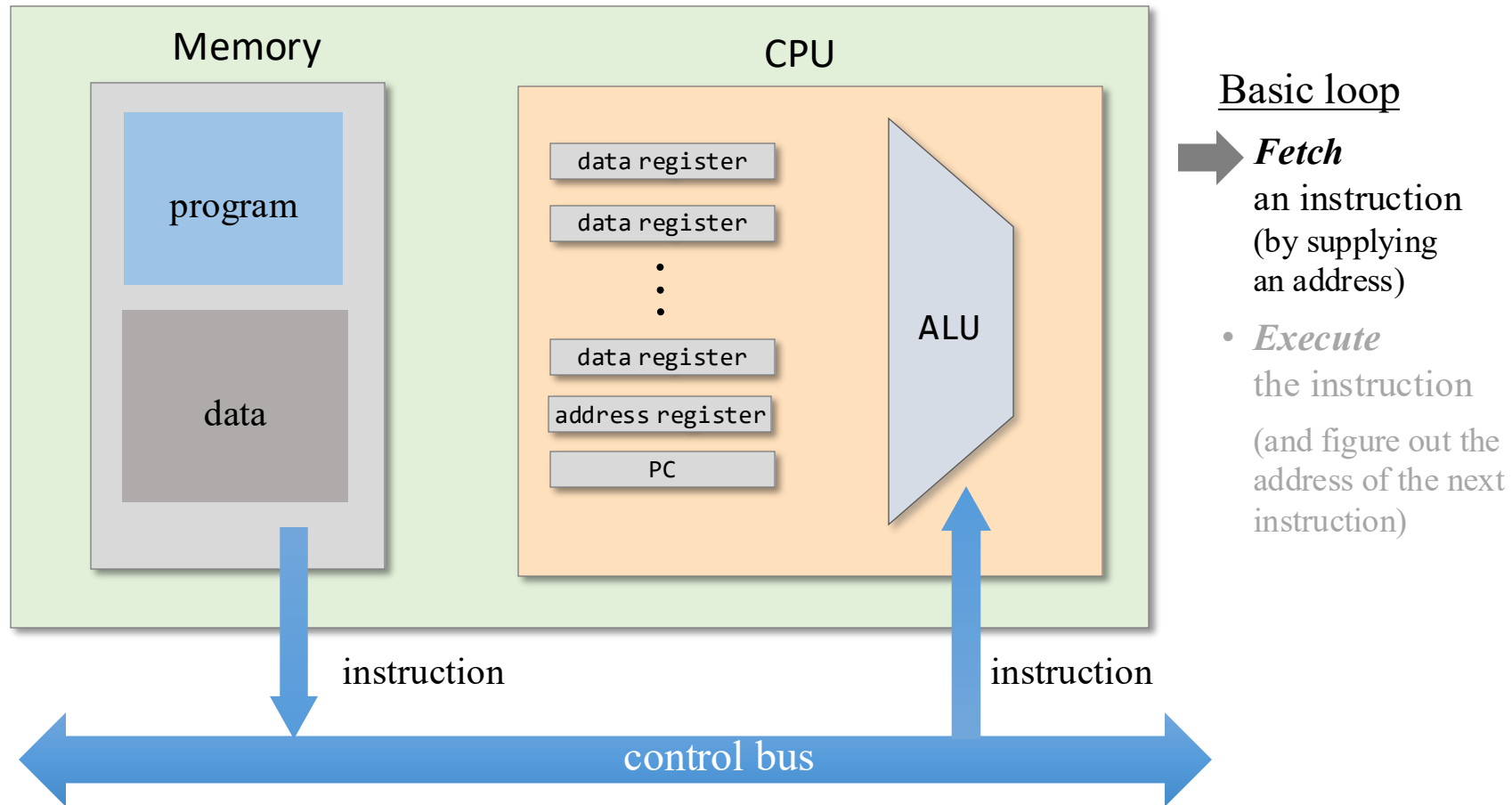


# Execute the instruction

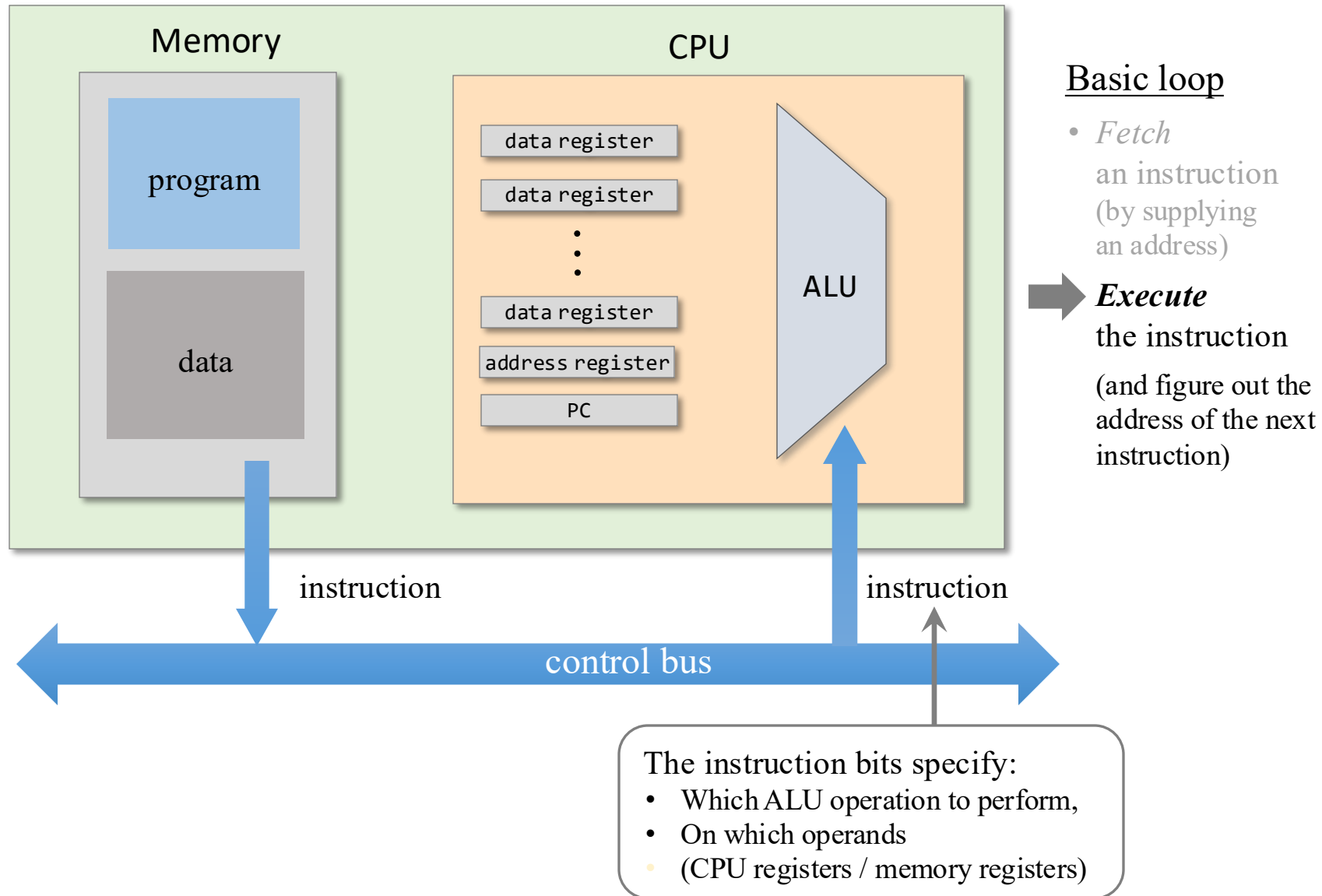





# Fetch – Execute issues

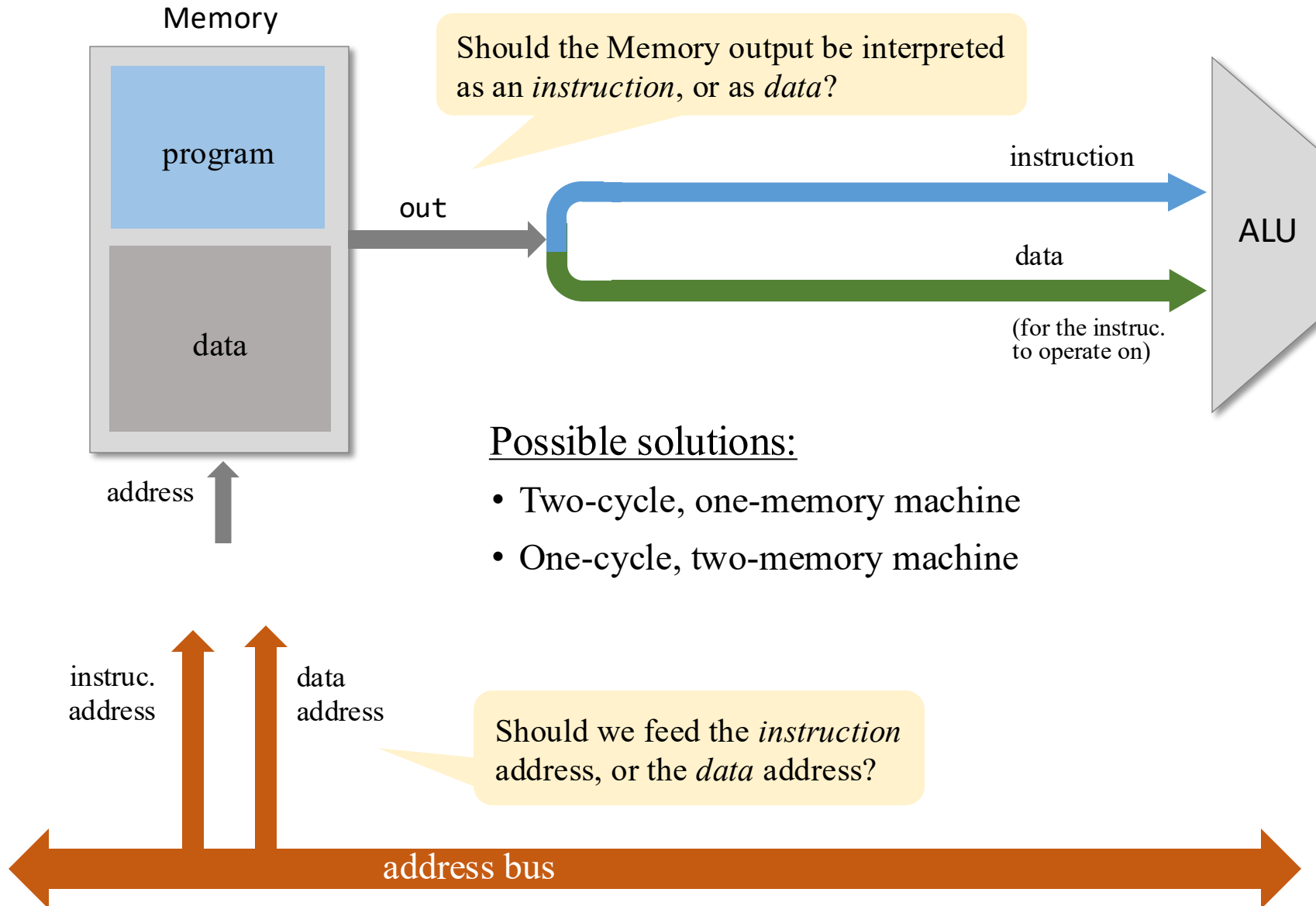


# Two-cycle, one-memory machine

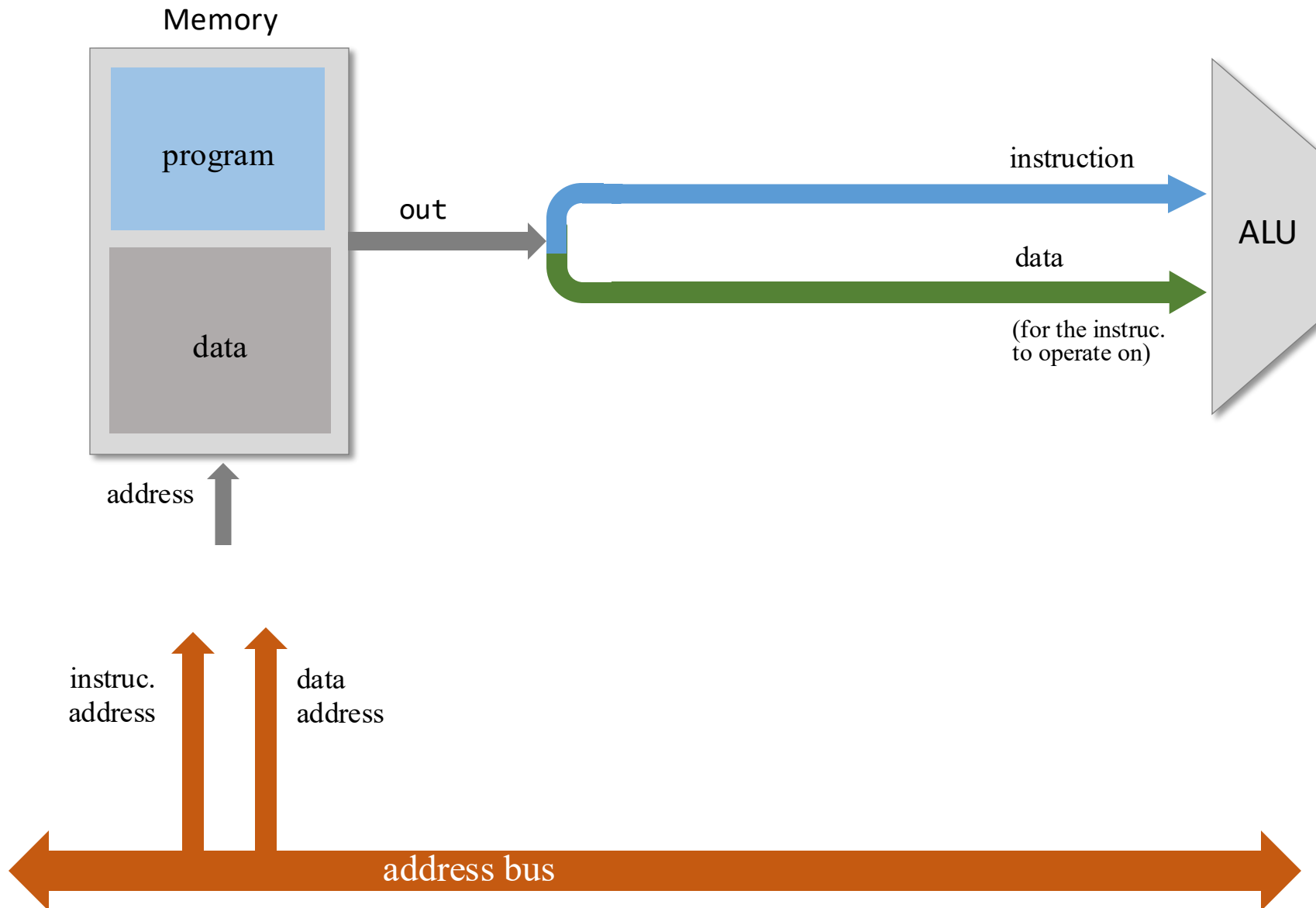

# Two-cycle, one-memory machine

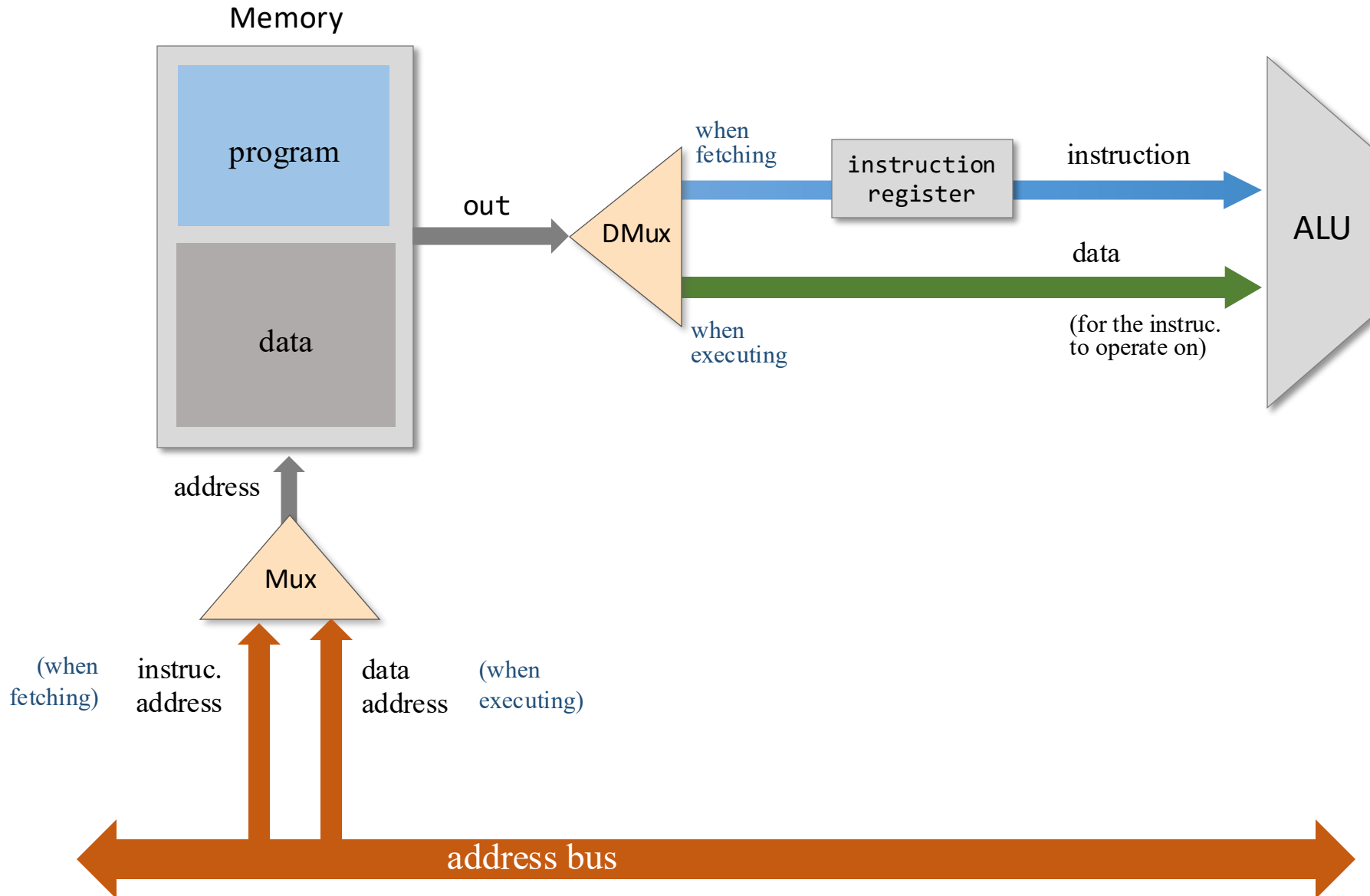


# Two-cycle, one-memory machine

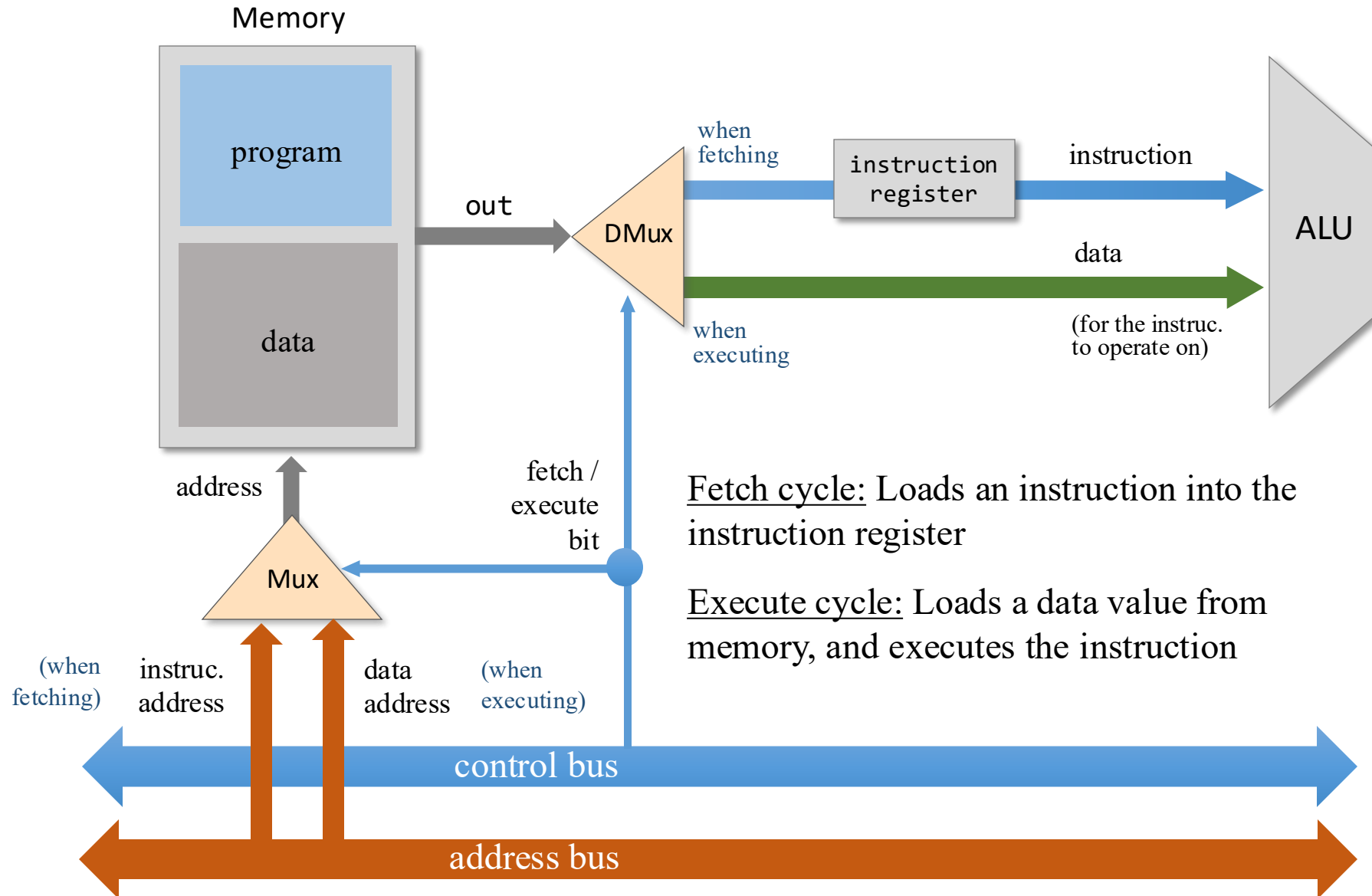

# Single cycle, two-memory machine


---

 

- Instructions and data are stored in two separate physical memories
  - Both memories are accessed simultaneously, in the same cycle
- (for historical reasons, referred to as "Harvard architecture")

# Single cycle, two-memory machine

---

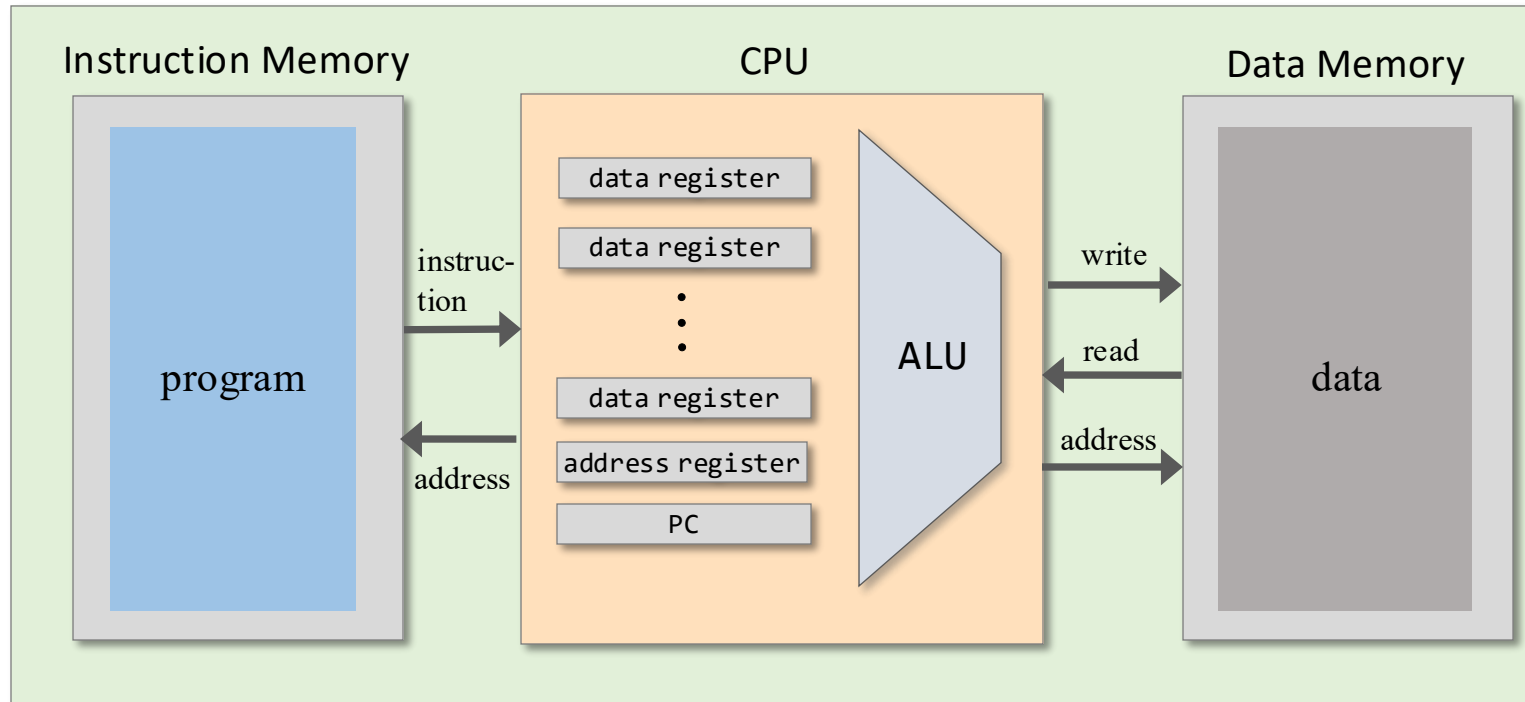

## Advantages

- Simple architecture
- Fast processing

## Disadvantages

- Two memory chips
- Separate address spaces

# Chapter 5: Computer Architecture

---

- ✓ Basic architecture
- ✓ Fetch-Execute cycle




## The Hack CPU

- Input / output

- Memory
- Computer
- Project 5: Chips
- Project 5: Guidelines

# The Hack computer

---

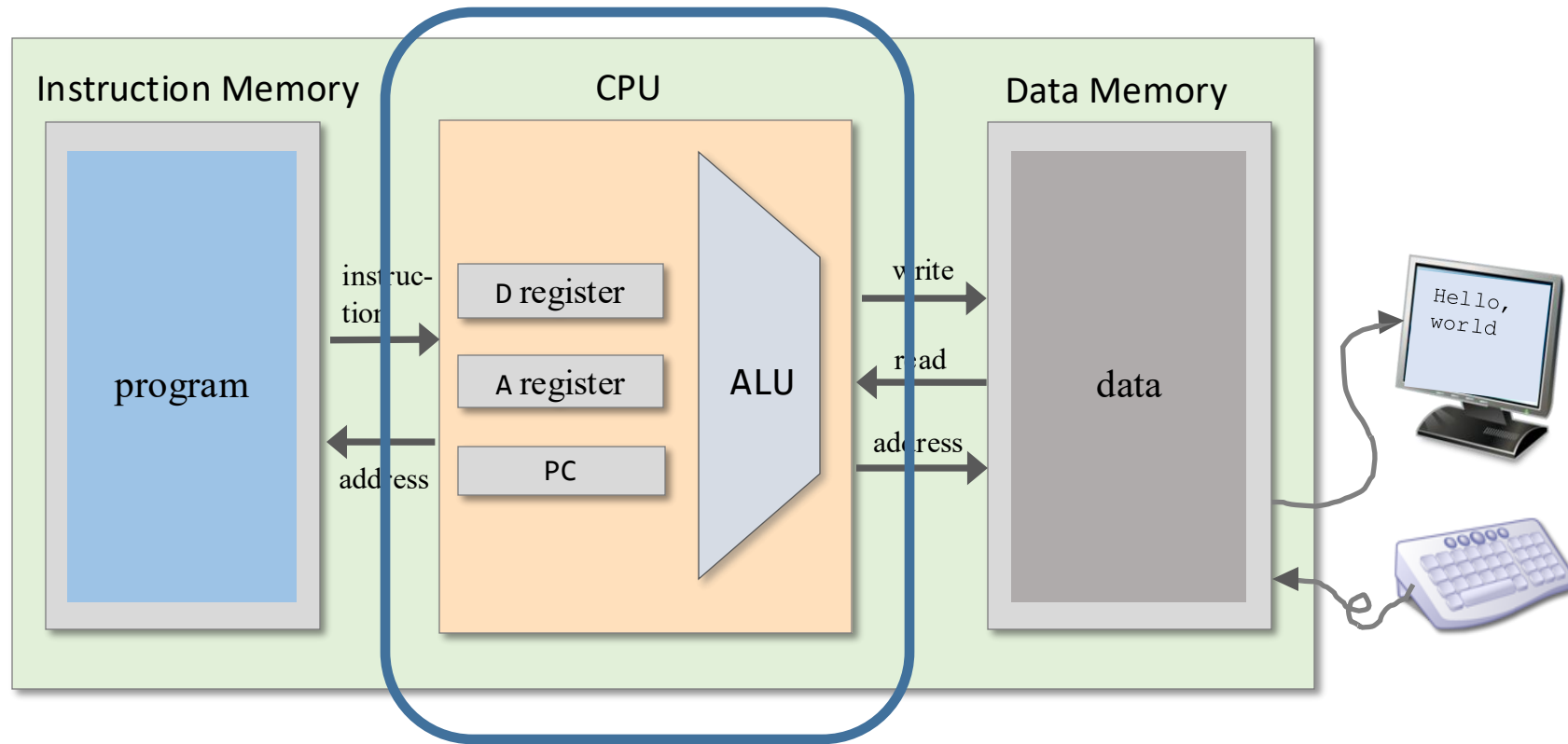



# CPU abstraction

A chip that implements the Hack instruction set:

A instruction      Symbolic:  $@xxx$       ( $xxx$  is a decimal value ranging from 0 to 32767, or a symbol bound to such a decimal value)  
                          Binary:  $0\ vvvvvvvvvvvvvvvv$       ( $vv \dots v = 15\text{-bit value of } xxx$ )


C instruction      Symbolic:  $dest = comp; jump$       ( $comp$  is mandatory.  
                          If  $dest$  is empty, the  $=$  is omitted;  
                          If  $jump$  is empty, the  $;$  is omitted)  
                          Binary:  $111a ccccc c d d j j j$

<i>comp</i>		<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>c</i>	<i>dest</i>	<i>d</i>	<i>d</i>	<i>d</i>	Effect: store <i>comp</i> in:
0		1	0	1	0	1	0	null	0	0	0	the value is not stored
1		1	1	1	1	1	1	M	0	0	1	RAM[A]
-1		1	1	1	0	1	0	D	0	1	0	D register (reg)
D		0	0	1	1	0	0	DM	0	1	1	RAM[A] and D reg
A	M	1	1	0	0	0	0	A	1	0	0	A reg
!D		0	0	1	1	0	1	AM	1	0	1	A reg and RAM[A]
!A	!M	1	1	0	0	0	1	AD	1	1	0	A reg and D reg
-D		0	0	1	1	1	1	ADM	1	1	1	A reg, D reg, and RAM[A]
-A	-M	1	1	0	0	1	1					
D+1		0	1	1	1	1	1					
A+1	M+1	1	1	0	1	1	1					
D-1		0	0	1	1	1	0					
A-1	M-1	1	1	0	0	1	0					
D+A	D+M	0	0	0	0	1	0					
D-A	D-M	0	1	0	0	1	1					
A-D	M-D	0	0	0	1	1	1					
D&A	D&M	0	0	0	0	0	0					
D A	D M	0	1	0	1	0	1					

$a == 0 \quad a == 1$

<i>jump</i>	<i>j</i>	<i>j</i>	<i>j</i>	Effect:
null	0	0	0	no jump
JGT	0	0	1	if <i>comp</i> > 0 jump
JEQ	0	1	0	if <i>comp</i> = 0 jump
JGE	0	1	1	if <i>comp</i> ≥ 0 jump
JLT	1	0	0	if <i>comp</i> < 0 jump
JNE	1	0	1	if <i>comp</i> ≠ 0 jump
JLE	1	1	0	if <i>comp</i> ≤ 0 jump
JMP	1	1	1	unconditional jump

# CPU abstraction

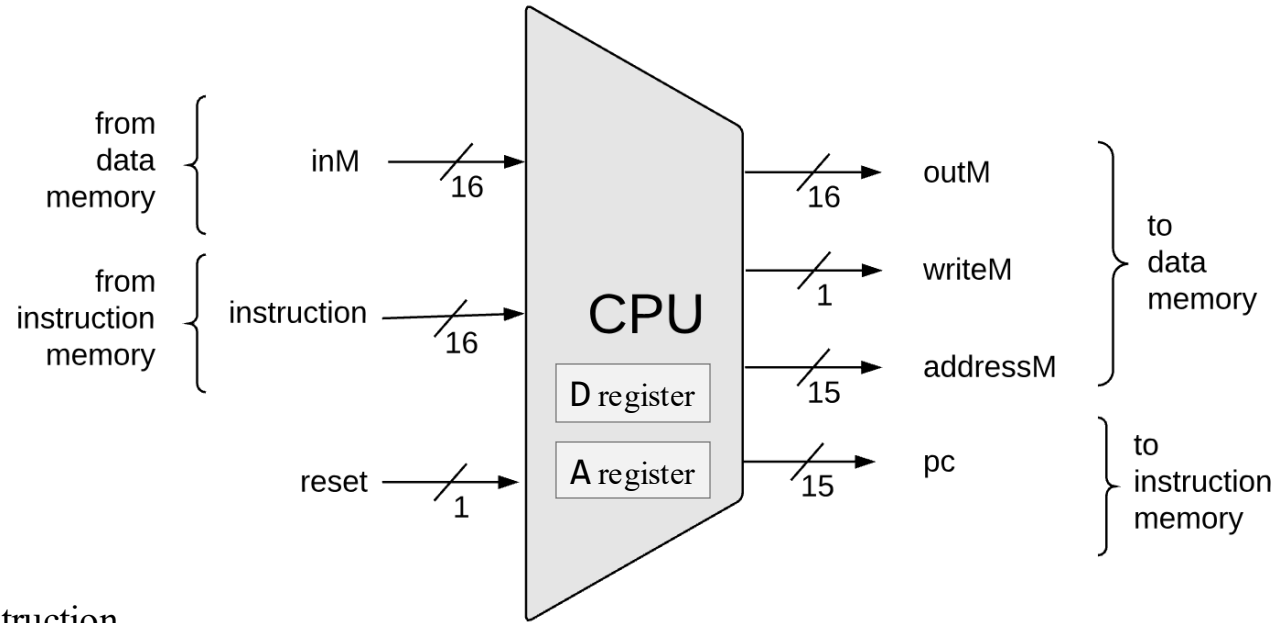


Instruction examples:

```
// D = RAM[5] + 1
@5
DM=M+1
...
// goto 200
@200
0;JMP
...
```

1. Executes the current instruction
2. Figures out which instruction to execute next

# CPU abstraction

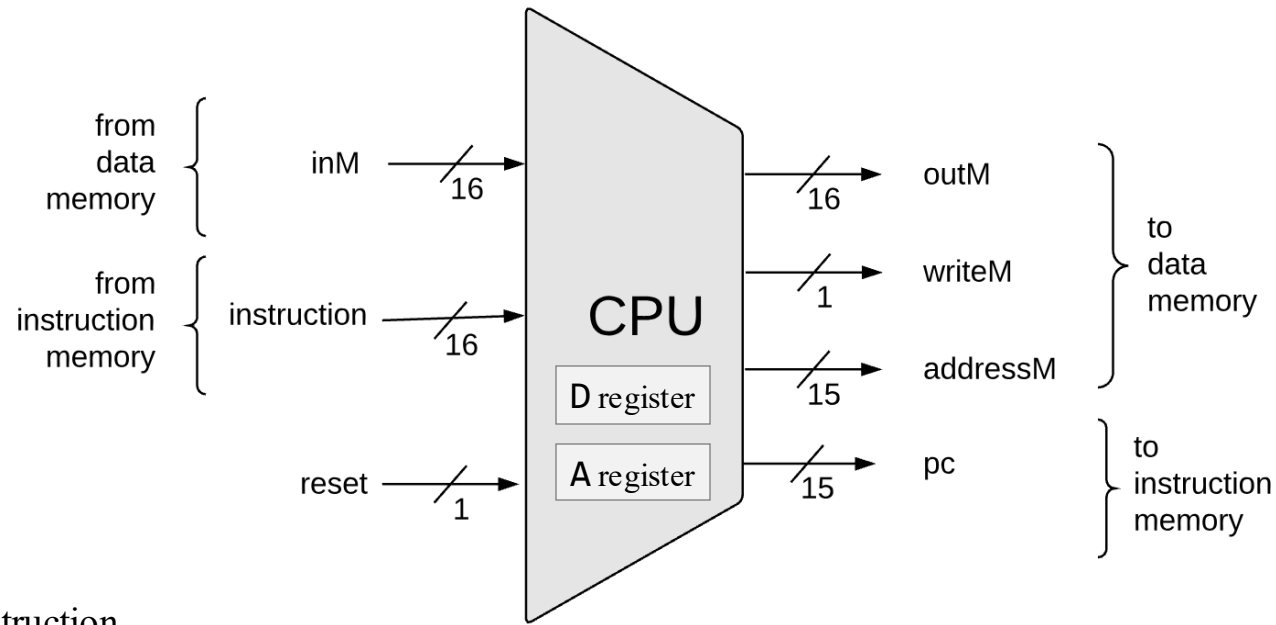

Instruction examples:

```
// D = RAM[5] + 1
@5
DM=M+1
...
// goto 200
@200
0; JMP
...
```


## 1. Executes the current instruction:

If it's an A-instruction (@xxx), sets the A register to xxx

Else (C-instruction):


- Computes the ALU function specified by the instruction (on the values of A, D, inM)
- Puts the ALU output in A, D, outM, as specified by the instruction
- If the instruction writes to M, sets addressM to A and asserts writeM

# CPU implementation

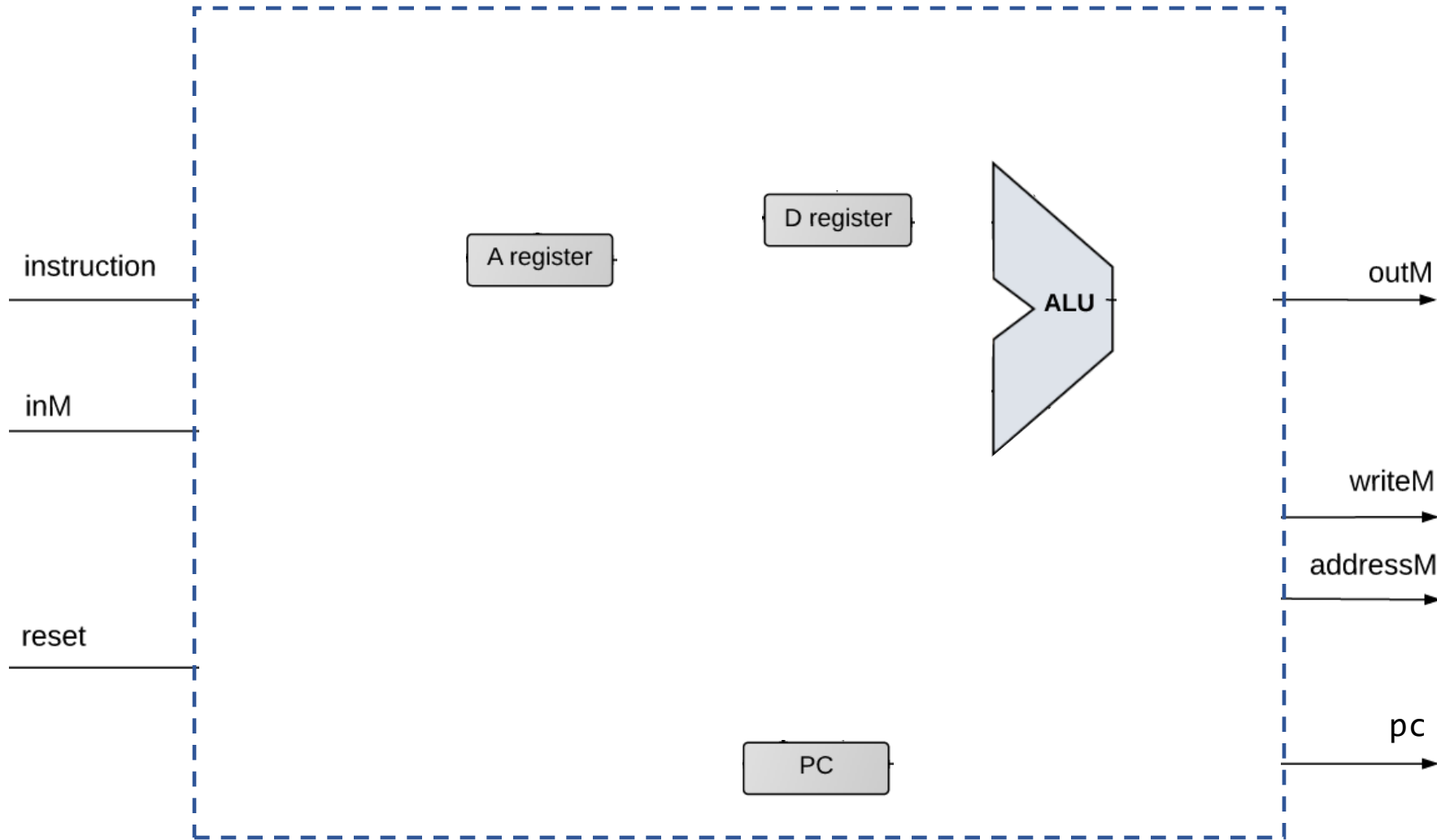


Hack CPU architecture

# CPU implementation

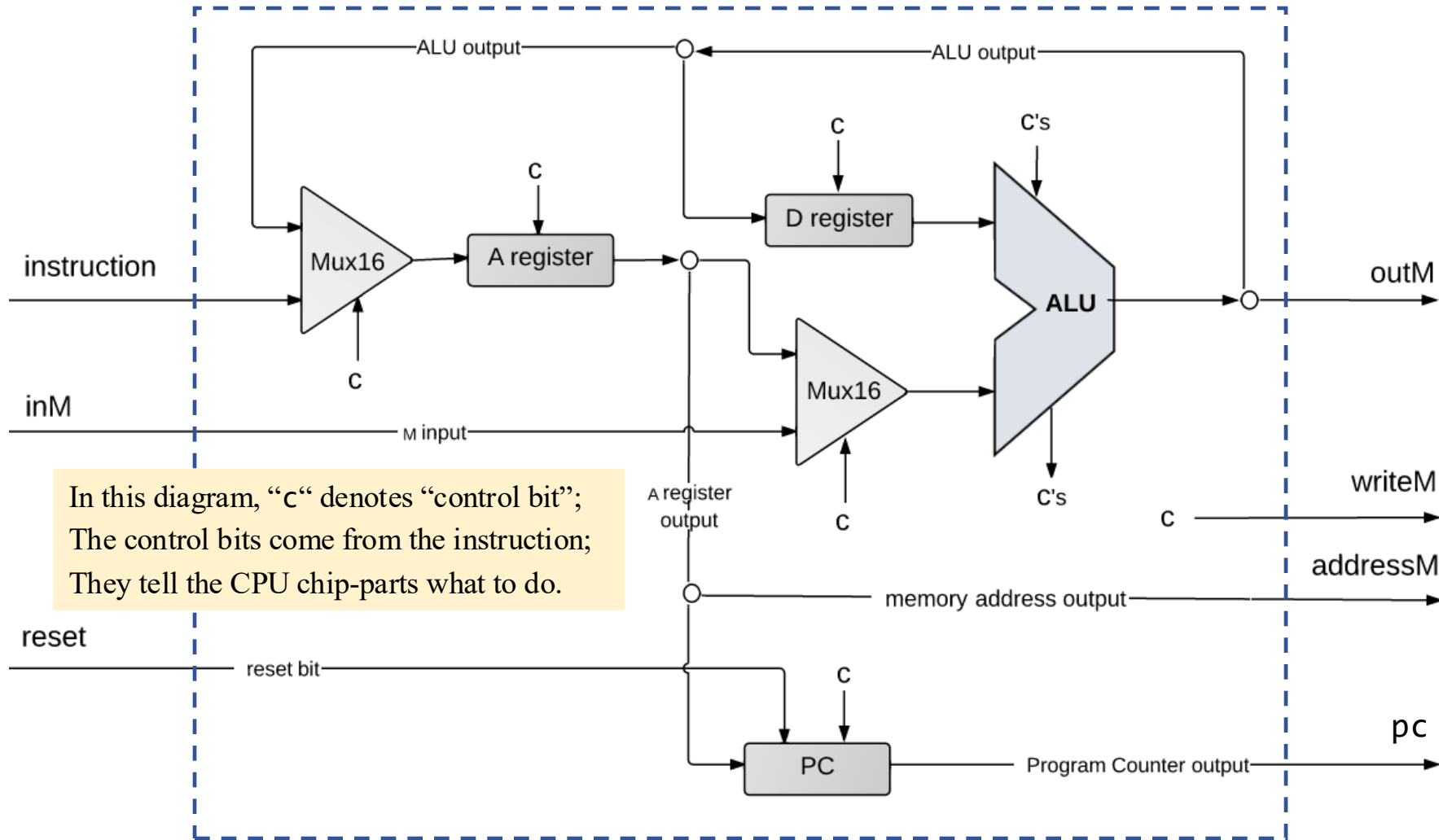


Hack CPU architecture
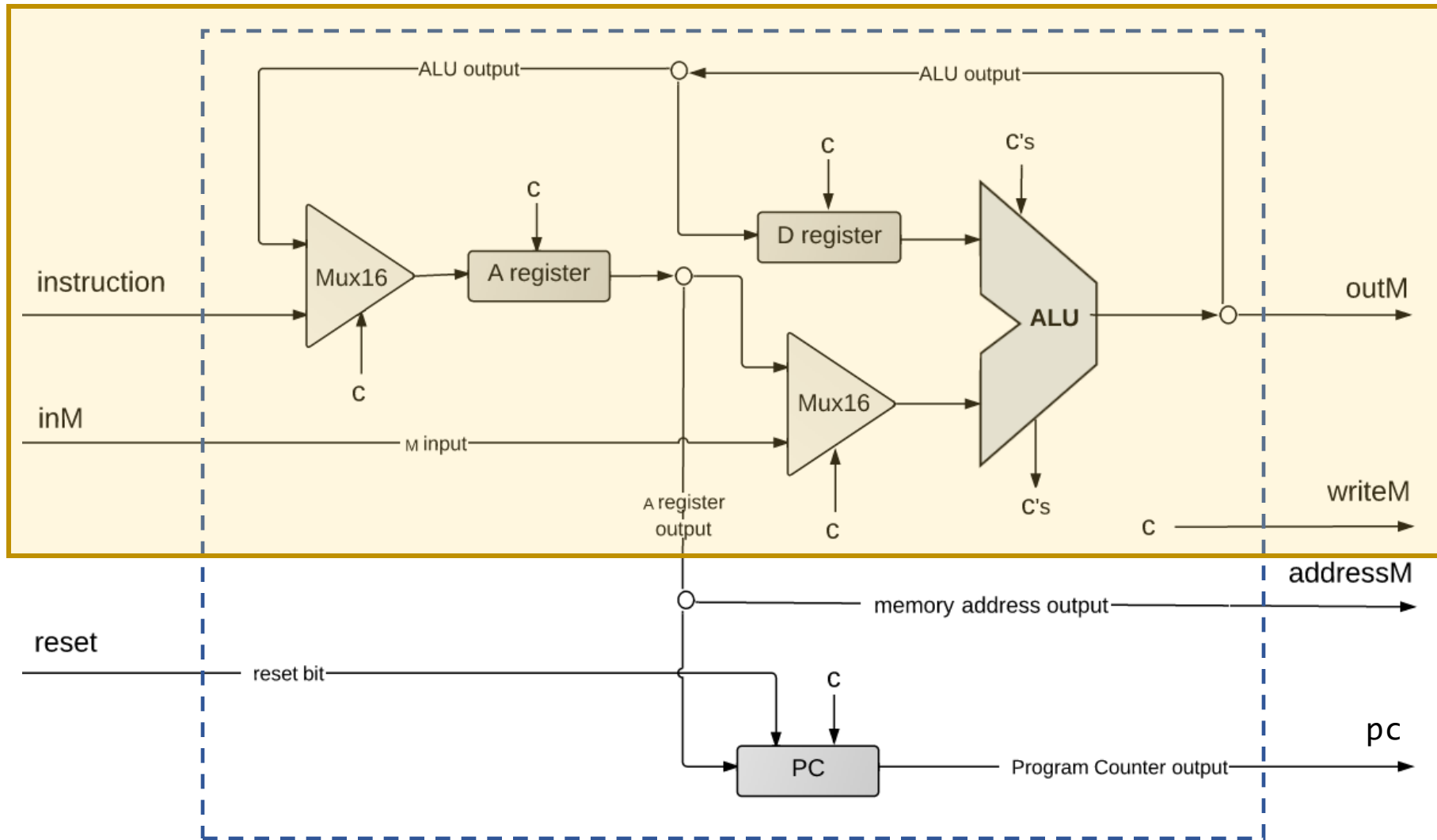
# CPU implementation: Instruction handling




Hack CPU architecture
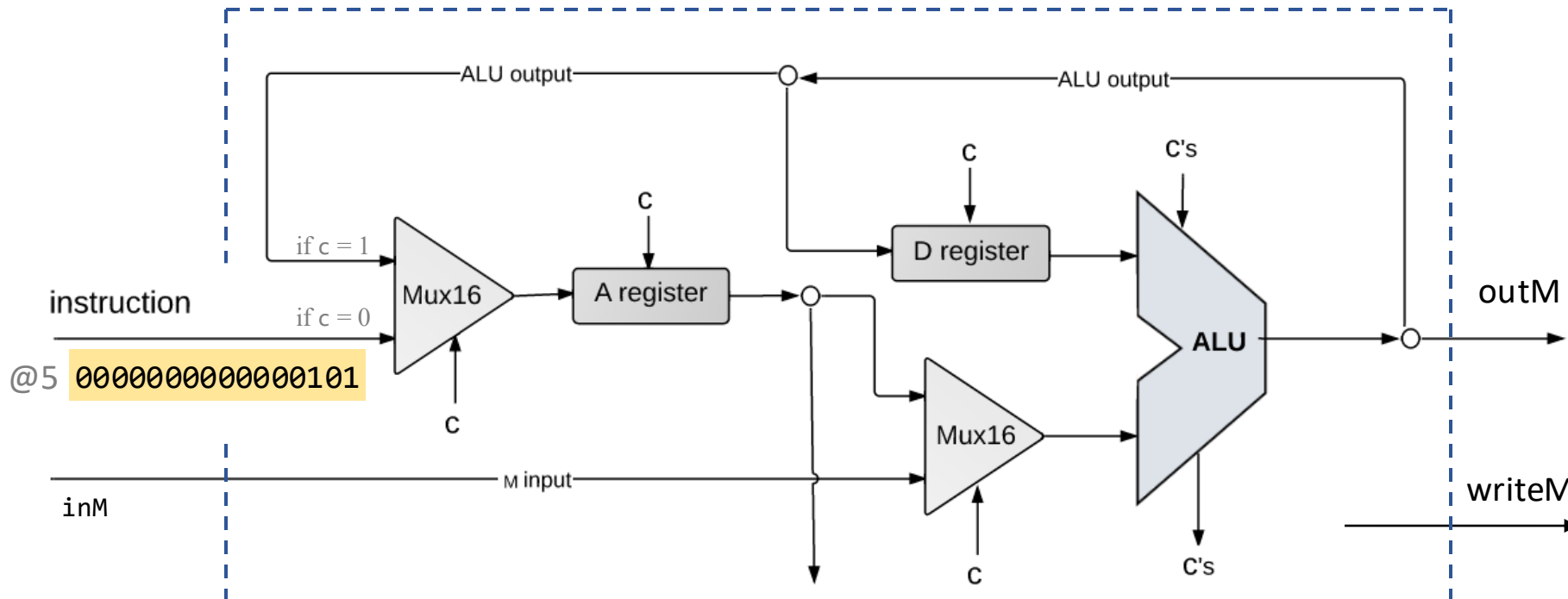
# CPU implementation: Instruction handling



## Handling A-instructions
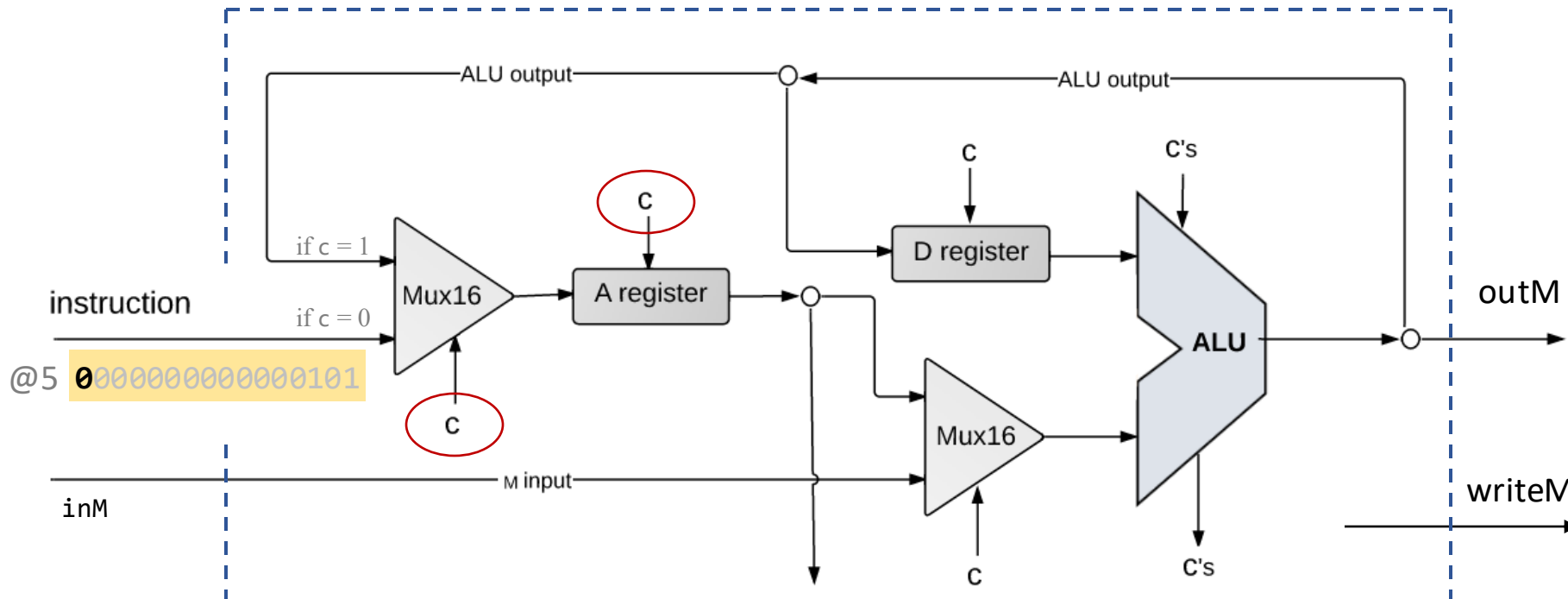
# CPU implementation: Instruction handling



## Handling A-instructions

Use the instruction's MSB (op-code) to manipulate the control bits of the A register and the Mux16 before it.






## Handling A-instructions

Use the instruction's MSB (op-code) to manipulate the control bits of the A register and the Mux16 before it.

**Effect: A-register  $\leftarrow$  instruction** (treated as a value)


(Exactly what the `@xxx` instruction specifies: “set A to `xxx`”)
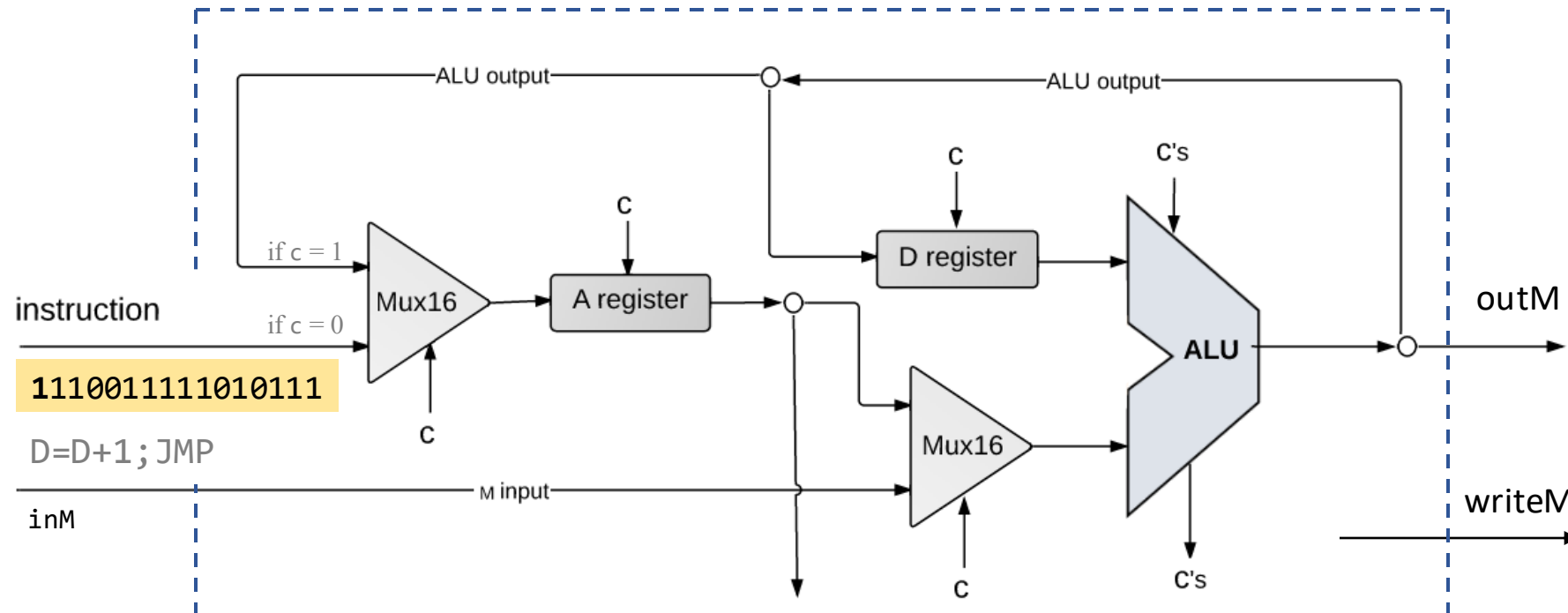
# CPU implementation: Instruction handling



## Handling C-instructions
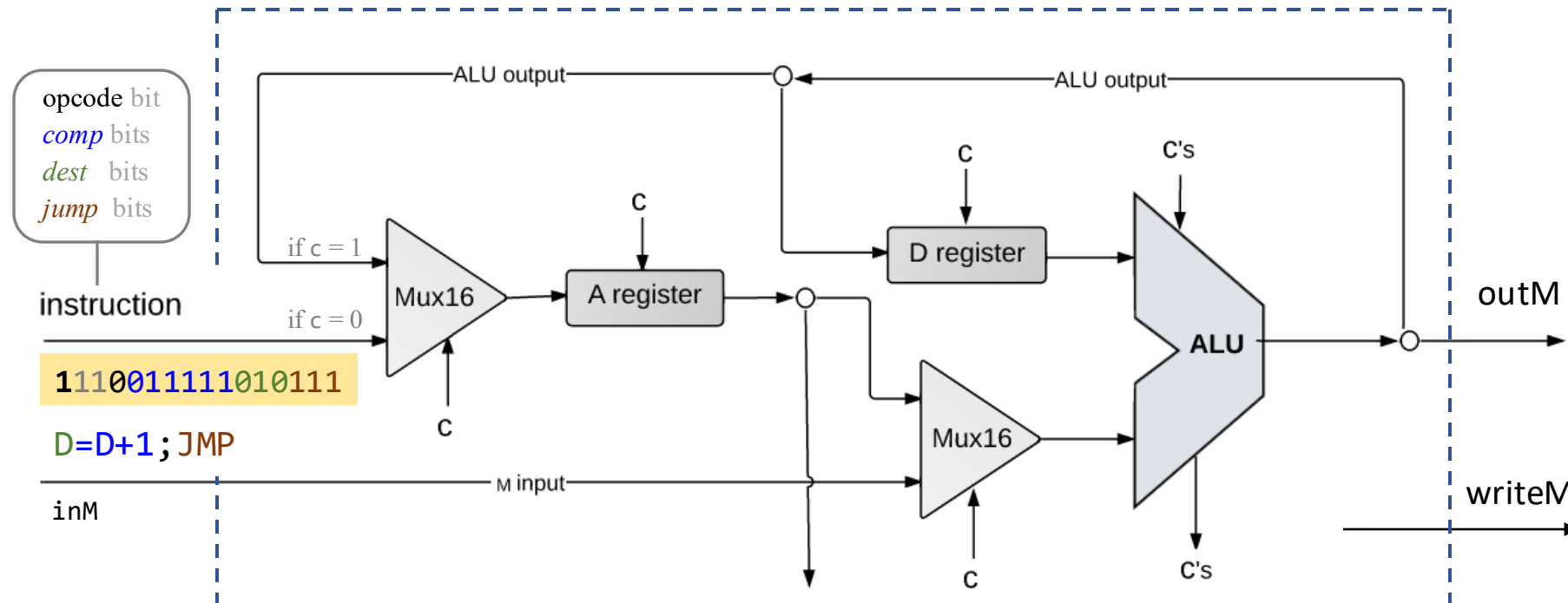
# CPU implementation: Instruction handling




## Handling C-instructions

Each instruction field (*opcode*, *comp*, *dest*, and *jump* bits) is handled separately

Each group of bits is used to "tell" a CPU chip-part what to do

Taken together, the chip-parts end up executing the instruction.

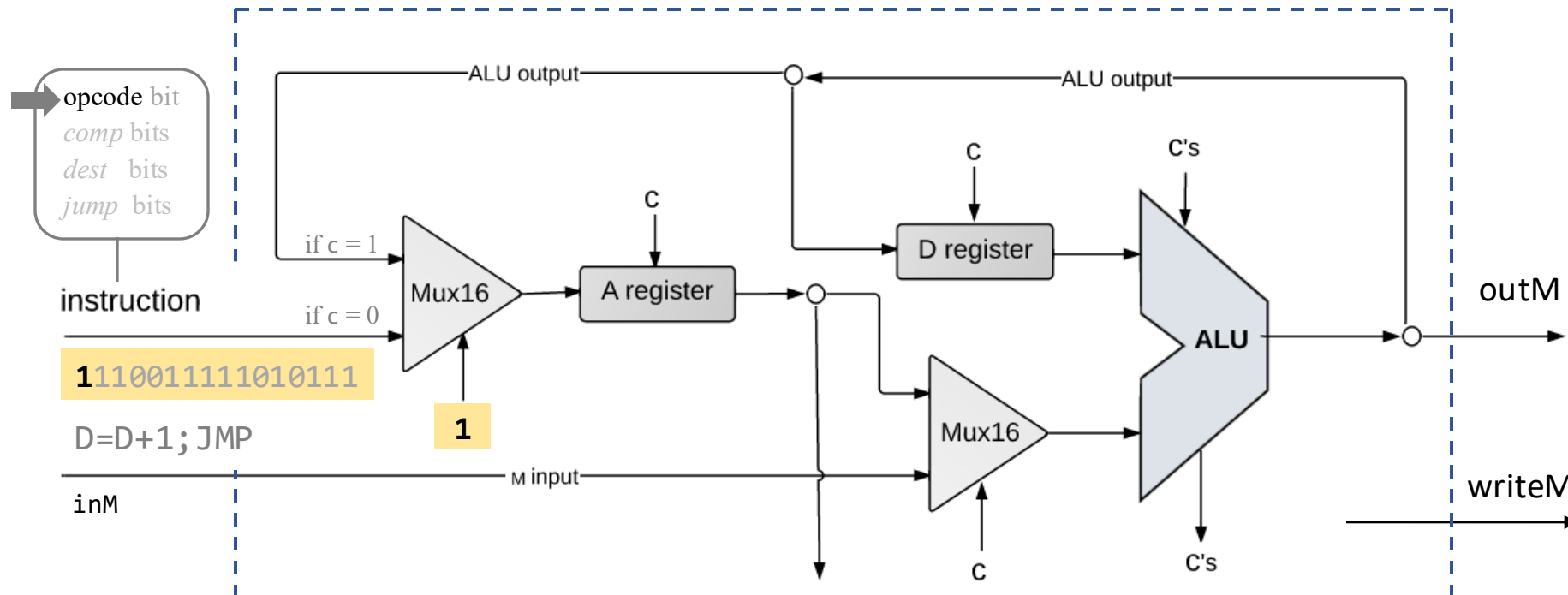
# CPU implementation: Instruction handling



Handling C-instructions: The *opcode* bit

Routes the instruction's MSB to the Mux16

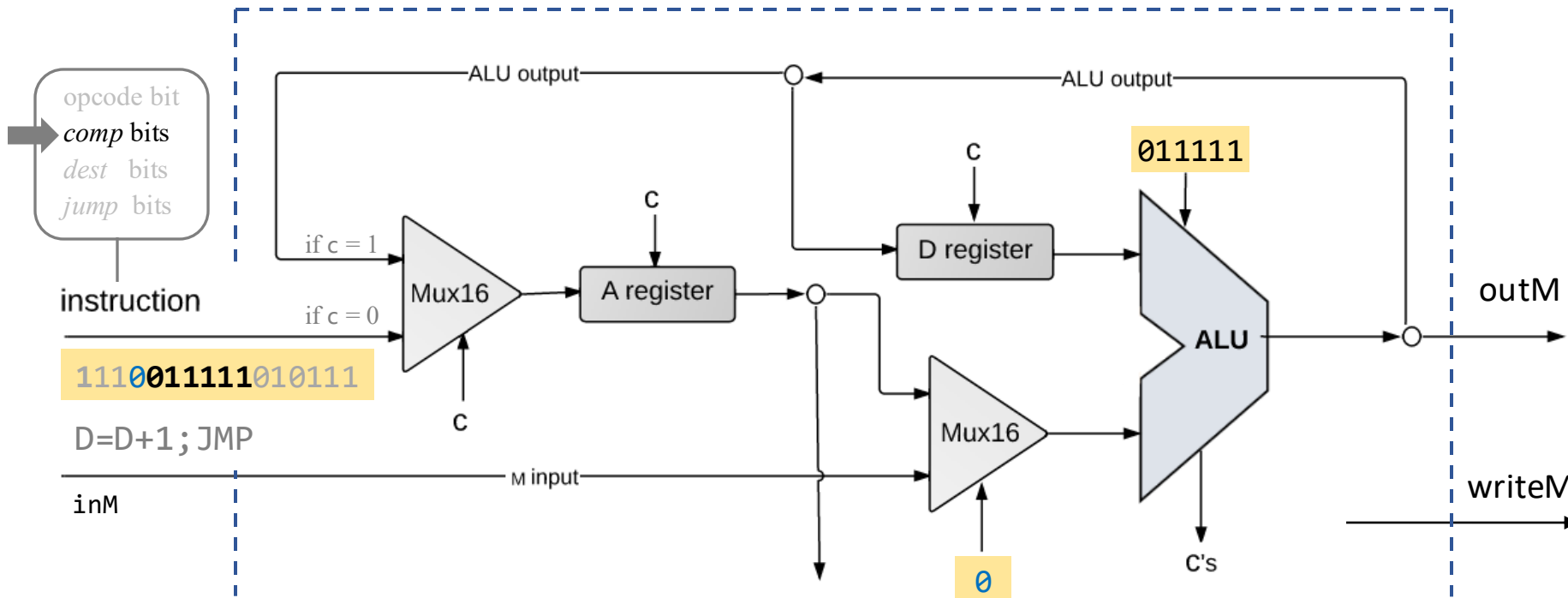**Effect: Primes the A register to get the ALU output.**




### Handling C-instructions: The *computation* bits

- Routes the instruction's c-bits to the ALU control bits
- Routes the instruction's a-bit to the Mux16

**Effect:** the ALU computes the specified function  
and emits the resulting value to the ALU output

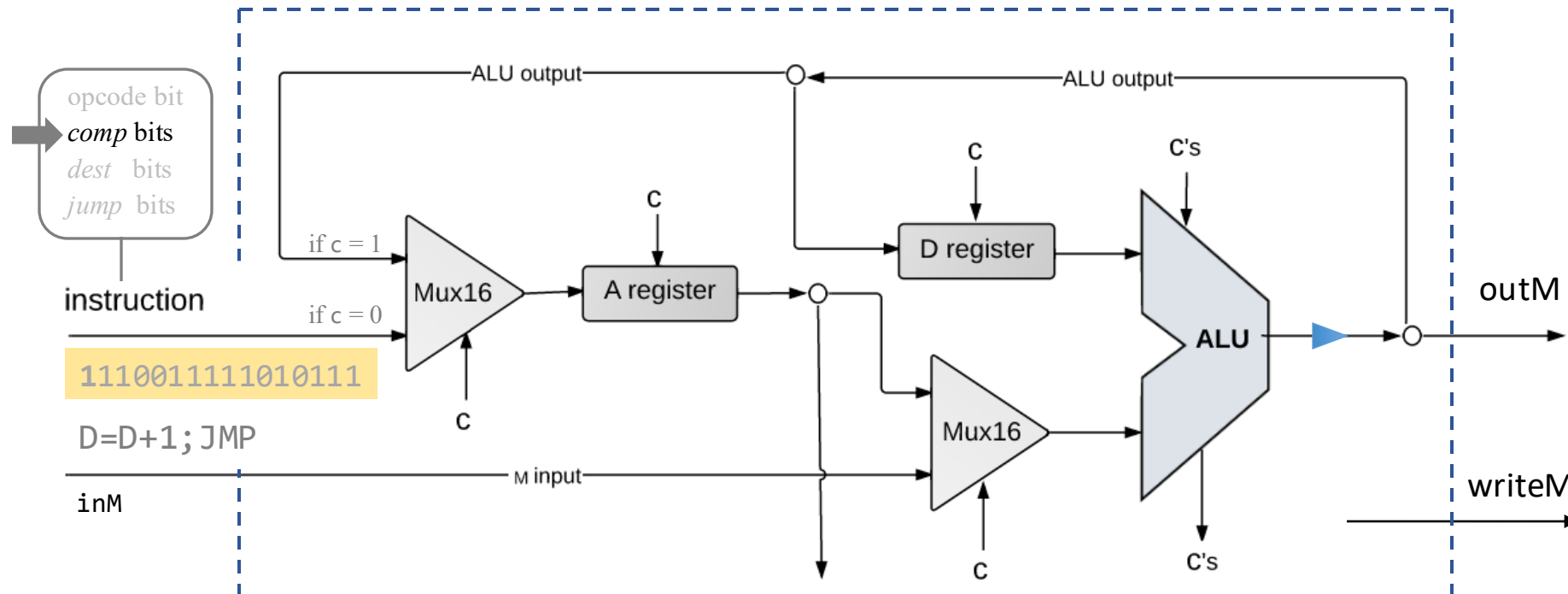
# CPU implementation: Instruction handling



ALU output:

- Result of ALU calculation

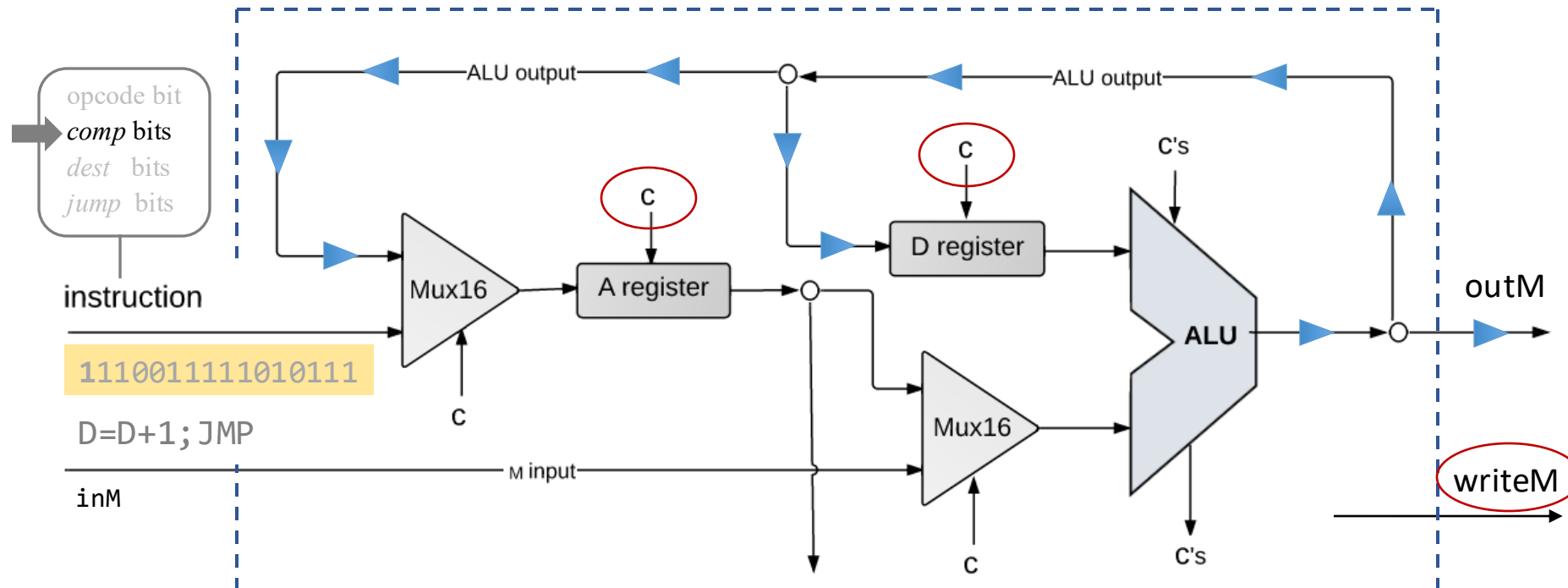
# CPU implementation: Instruction handling



ALU output:

- Result of ALU calculation
- Fed simultaneously to D-register, A-register, data memory
- Each enabled/disabled by its control bit

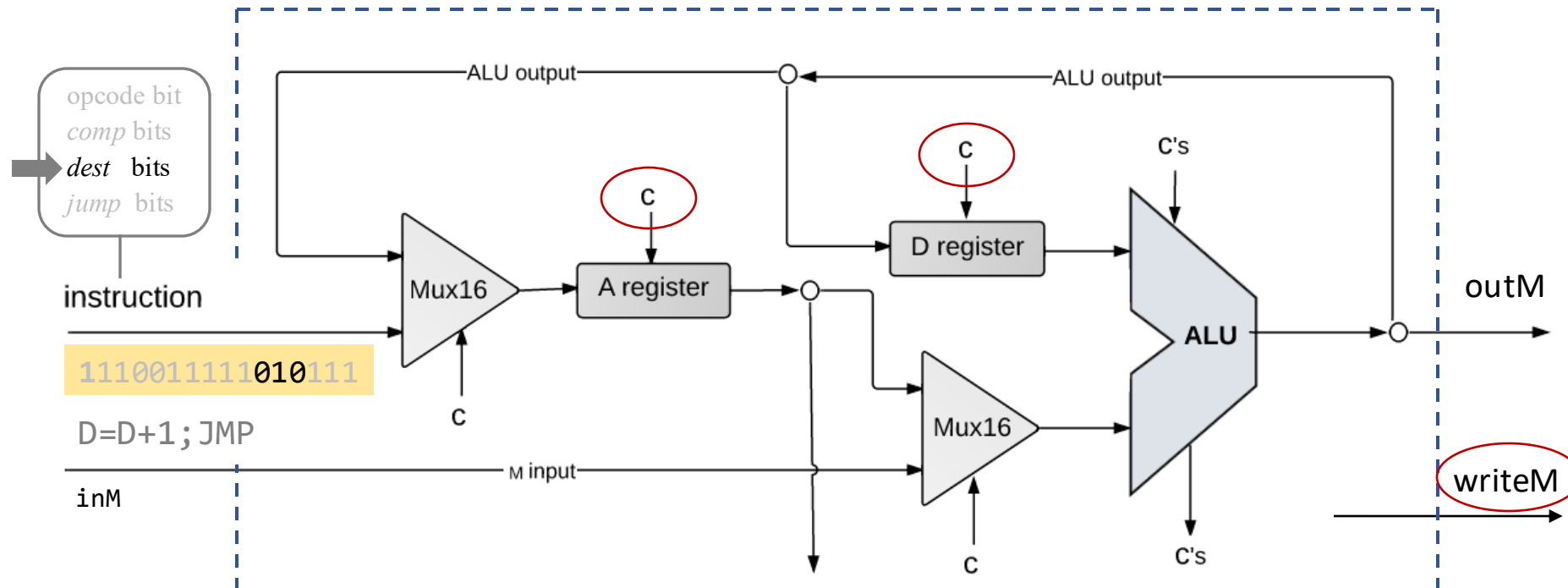
# CPU implementation: Instruction handling



Handling C-instructions: The *destination* bits


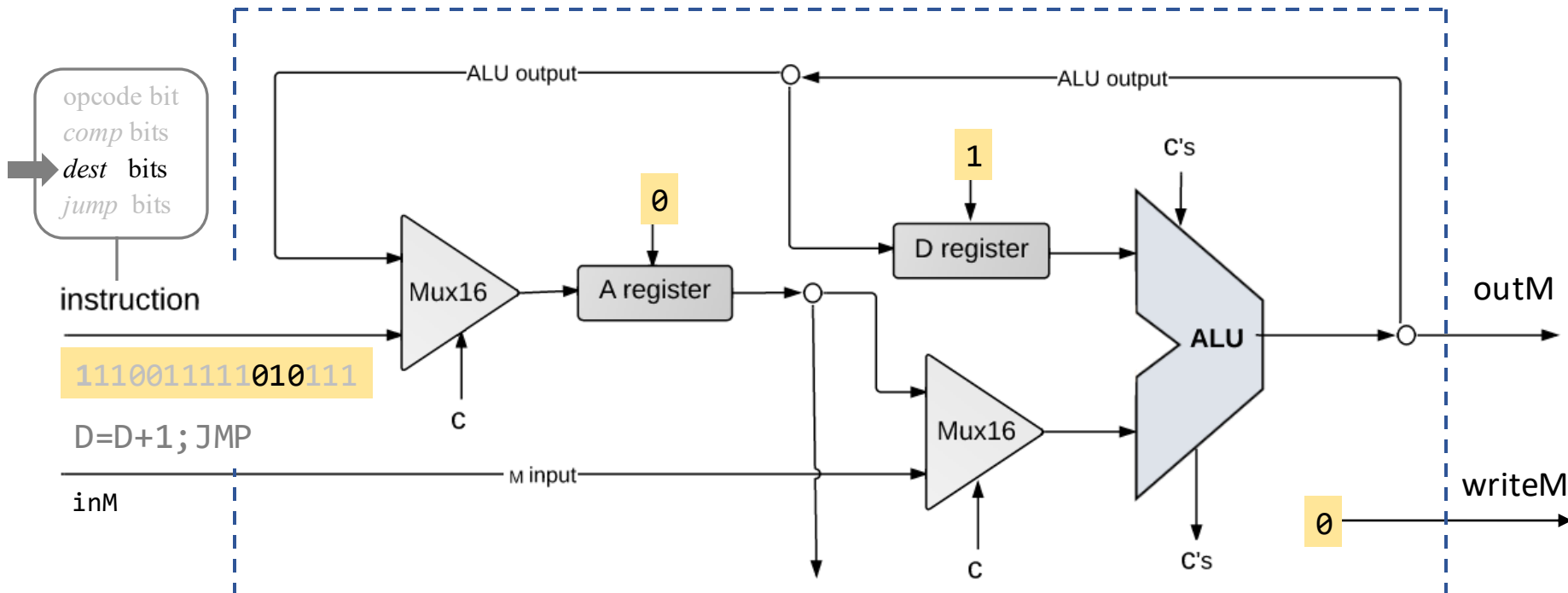
# CPU implementation: Instruction handling




## Handling C-instructions: The *destination* bits

Routes the instruction's d-bits to the control (load) bits of the A-register, D-register, and to the writeM bit

**Effect: Only the enabled destinations commit to the ALU output**

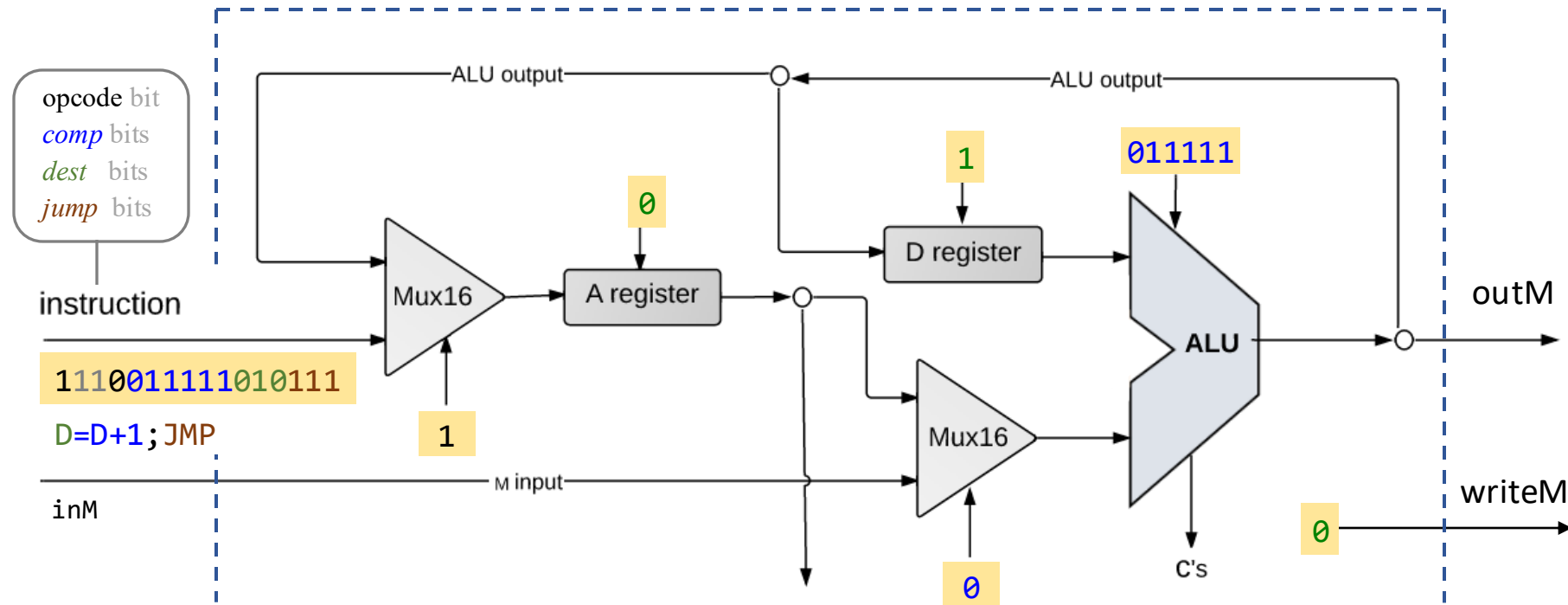
# CPU implementation: Instruction handling



## Handling C-instructions: Recap


- ✓ Executes *dest* = *comp*
- ➔ Figures out which instruction to execute next

# CPU implementation: Control

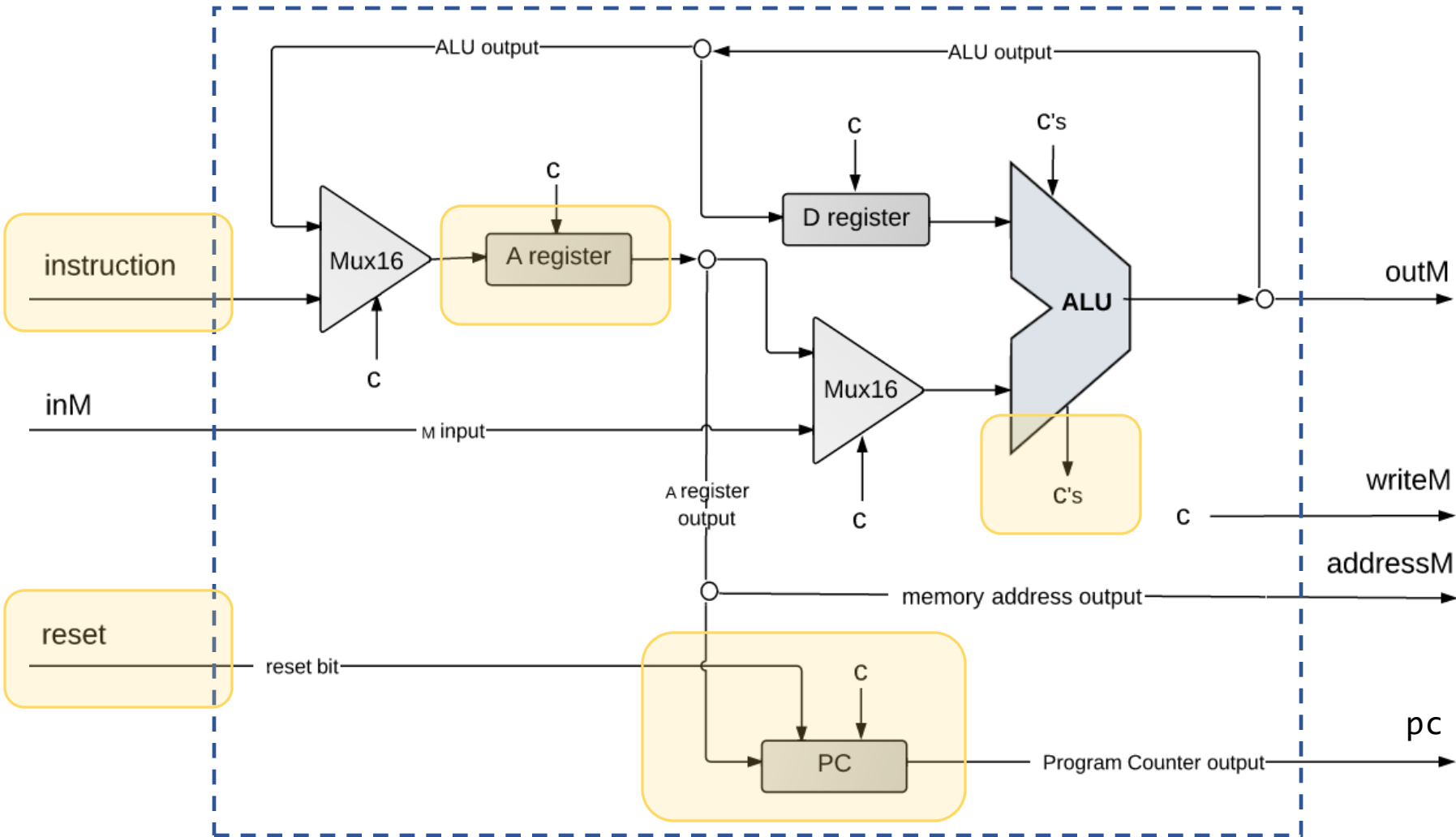

Hack CPU architecture

# CPU implementation: Control

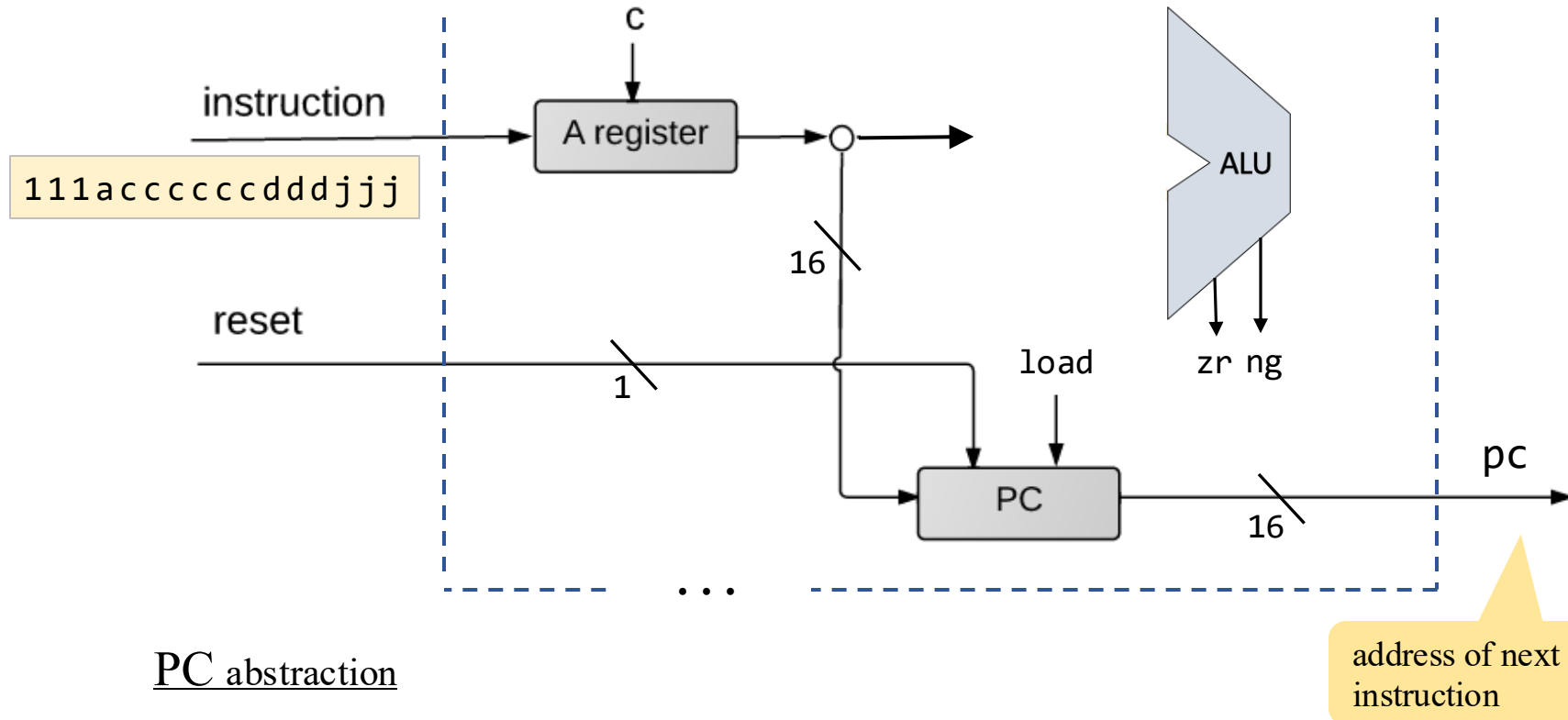

## PC abstraction


Outputs the address of the next instruction, has three states:

*reset:*  $PC \leftarrow 0$

*no jump:*  $PC++$

*jump:*  $\text{if } (condition) PC \leftarrow A$  // Note: A was already set to the jump address

# CPU implementation: Control

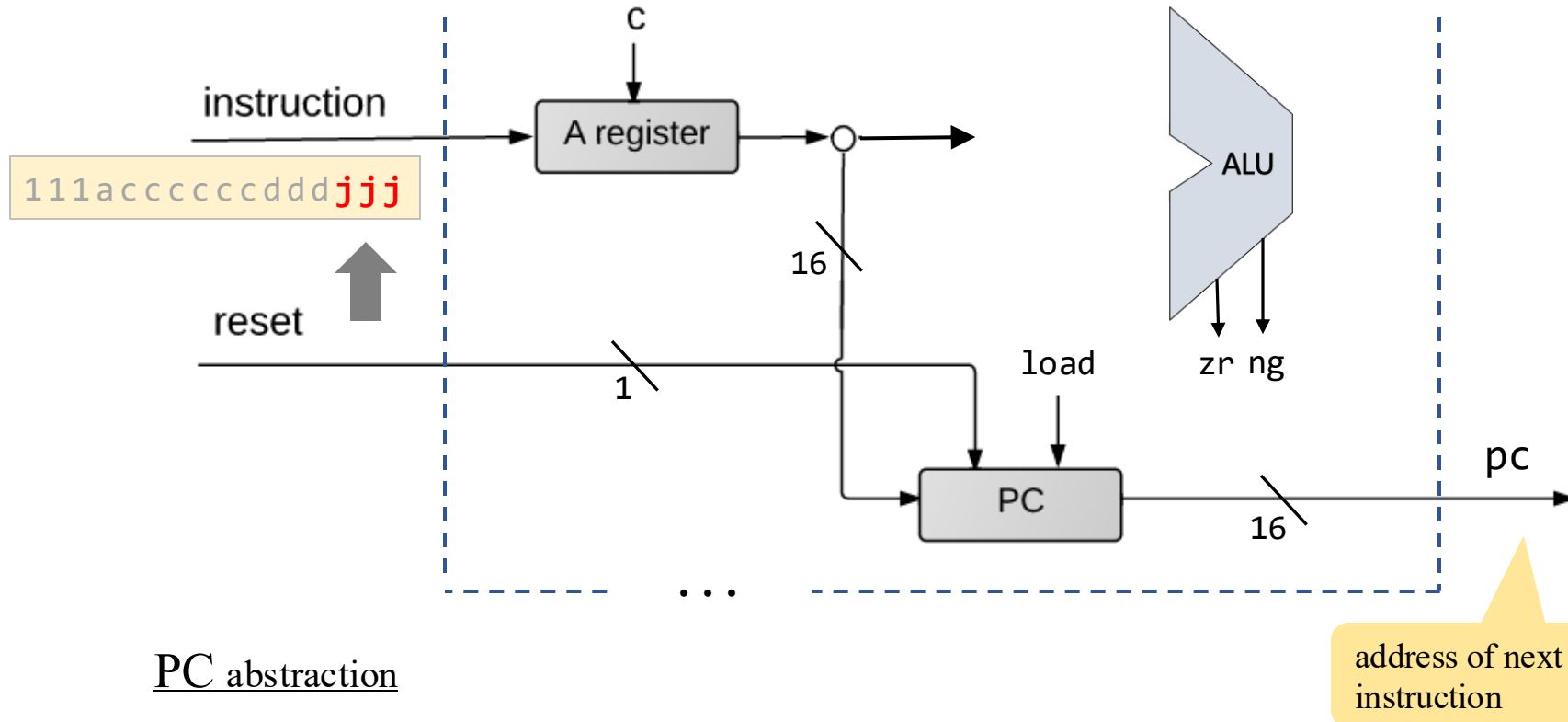

## PC abstraction

Outputs the address of the next instruction, has three states:

*reset:*  $PC \leftarrow 0$

*no jump:*  $PC++$

*jump:*  $\text{if } (condition) PC \leftarrow A$  // Note: A was already set to the jump address

# CPU implementation: Control


Symbolic  
syntax:

*dest = comp ; jump*

Binary  
syntax:

1 1 1 a c c c c c c d d d j1 j2 j3


<i>jump</i>	j1	j2	j3	<i>condition</i>
null	0	0	0	no jump
JGT	0	0	1	if (ALU out > 0) jump
JEQ	0	1	0	if (ALU out = 0) jump
JGE	0	1	1	if (ALU out ≥ 0) jump
JLT	1	0	0	if (ALU out < 0) jump
JNE	1	0	1	if (ALU out ≠ 0) jump
JLE	1	1	0	if (ALU out ≤ 0) jump
JMP	1	1	1	Unconditional jump

 


We can use gate logic to compute:

$J(j1, j2, j3, zr, ng) = 1$  if *condition* is true  
0 otherwise

# CPU implementation: Control

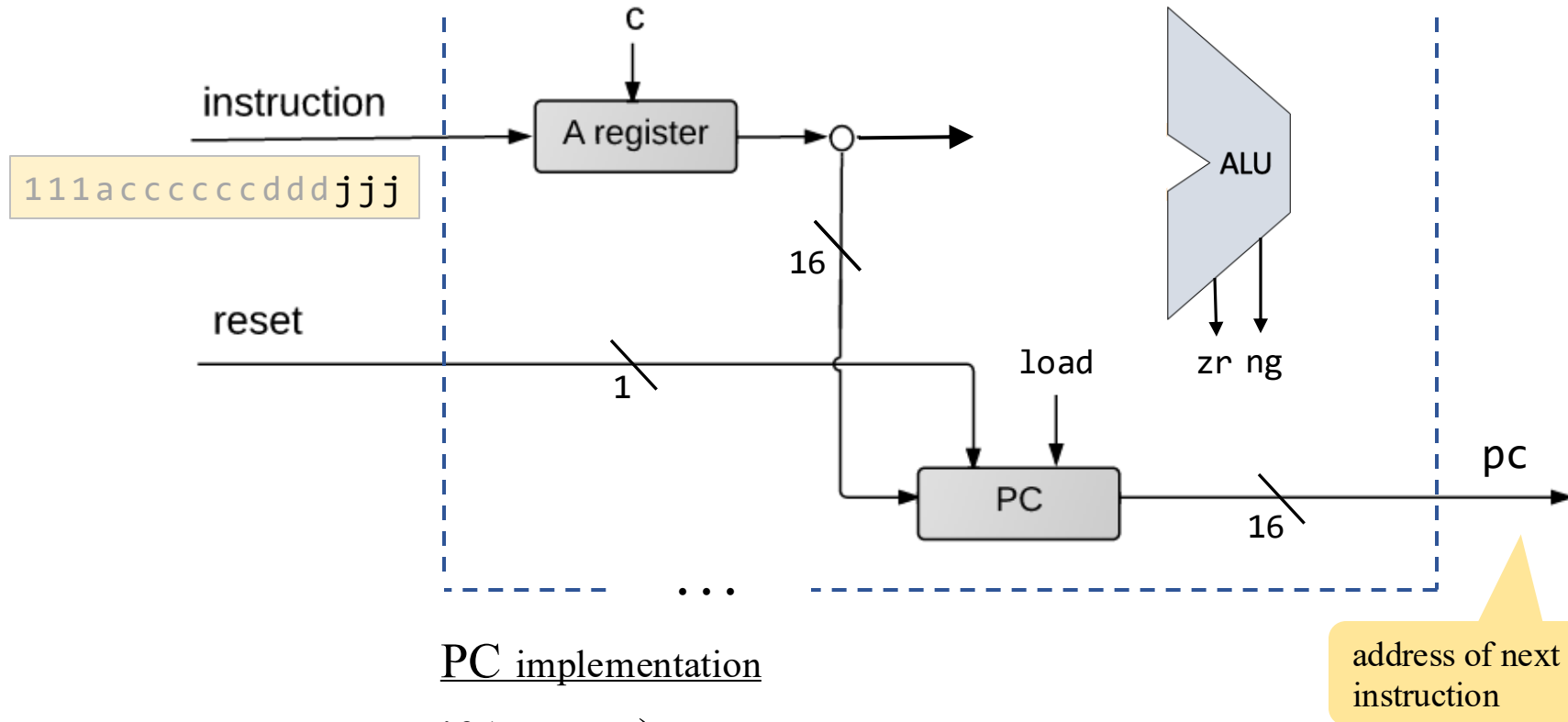

# CPU implementation

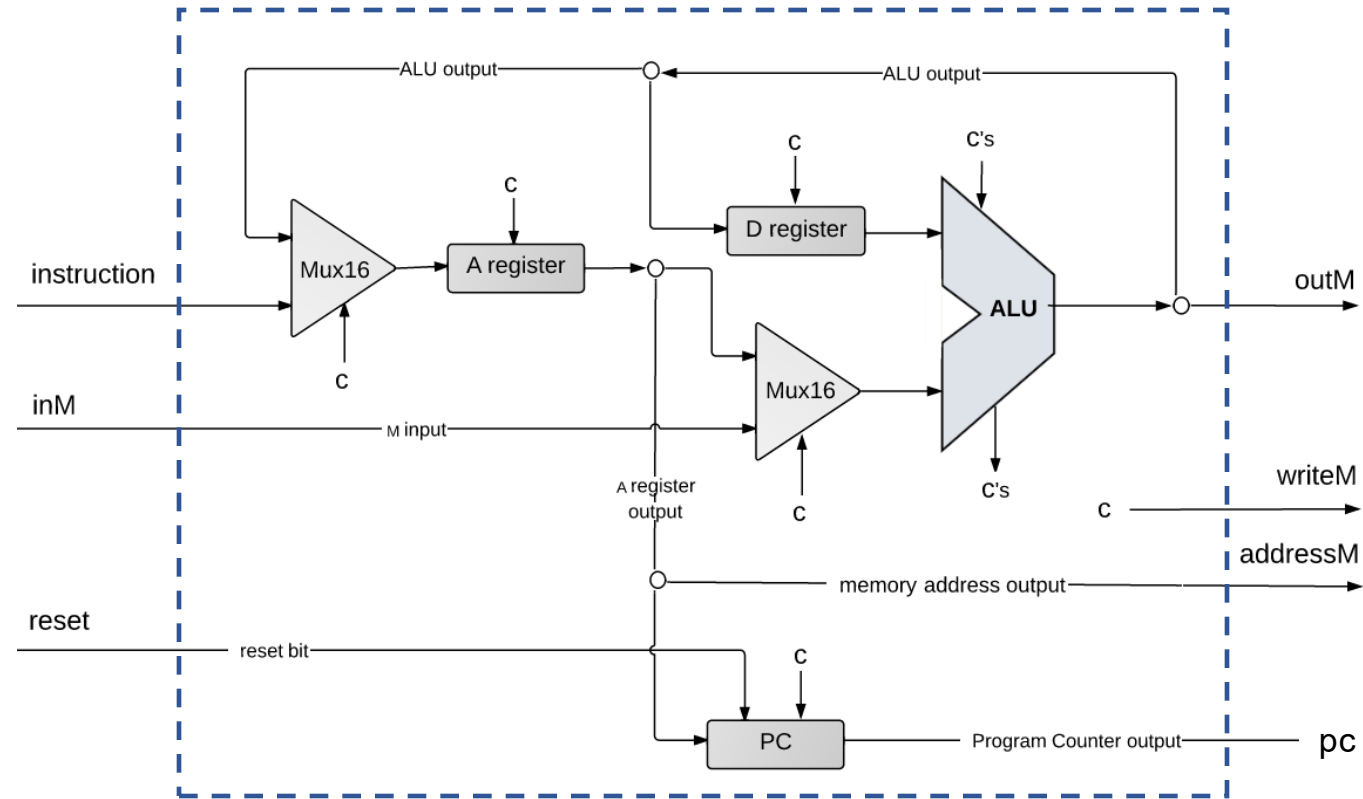

Executes the current instruction



Figures out which instruction to execute next.




# Computer Architecture

---


- ✓ Basic architecture
  - ✓ Fetch-Execute cycle
  - ✓ The Hack CPU
  - ➡ Input / output
- Memory
  - Computer
  - Project 5: Chips
  - Project 5: Guidelines

# Hack computer

---

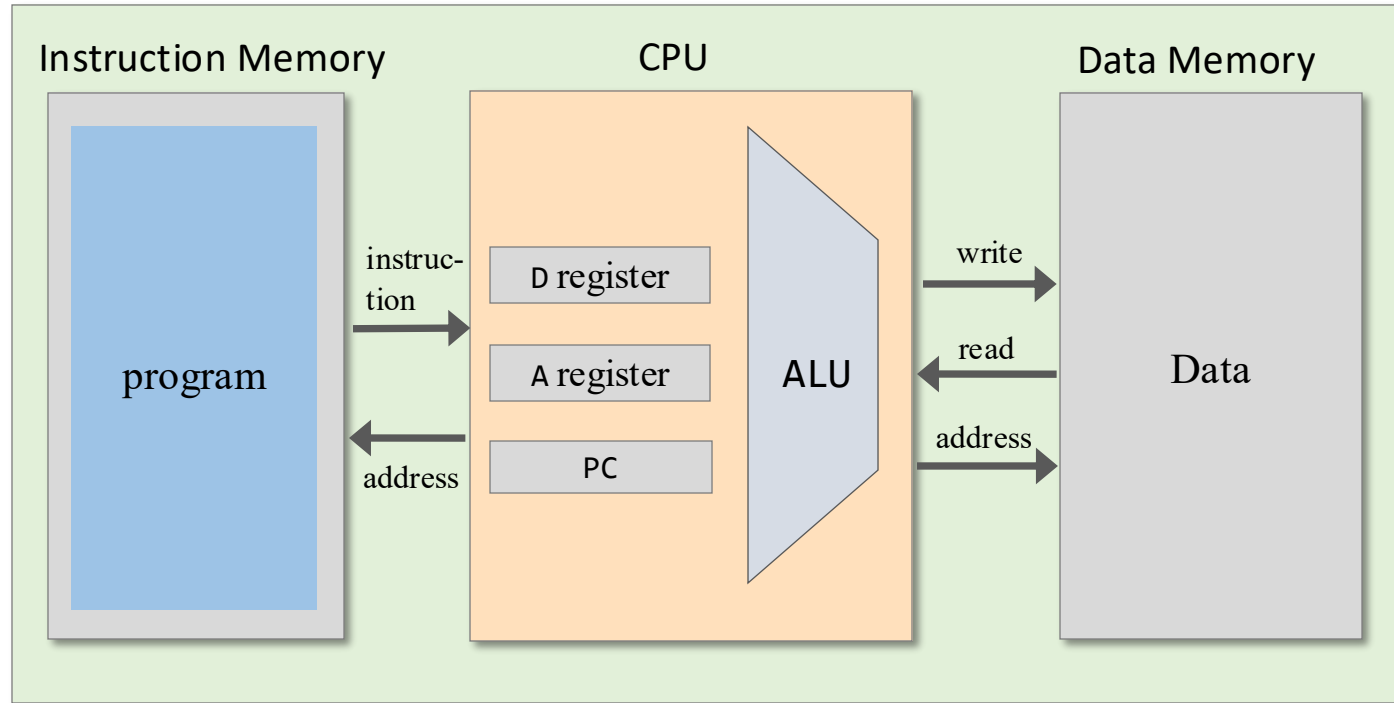


# Hack computer

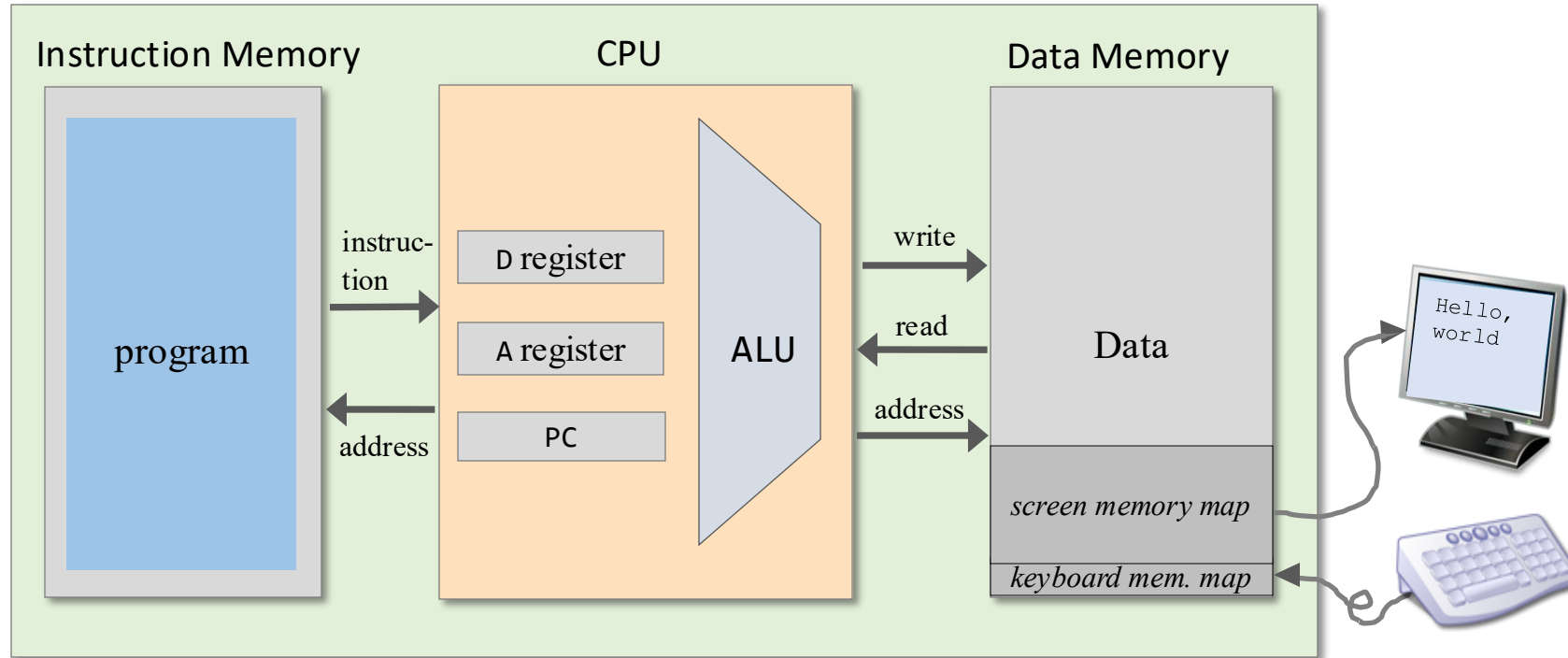


## I/O devices

- Screen
- Keyboard


# Screen

 


# Screen

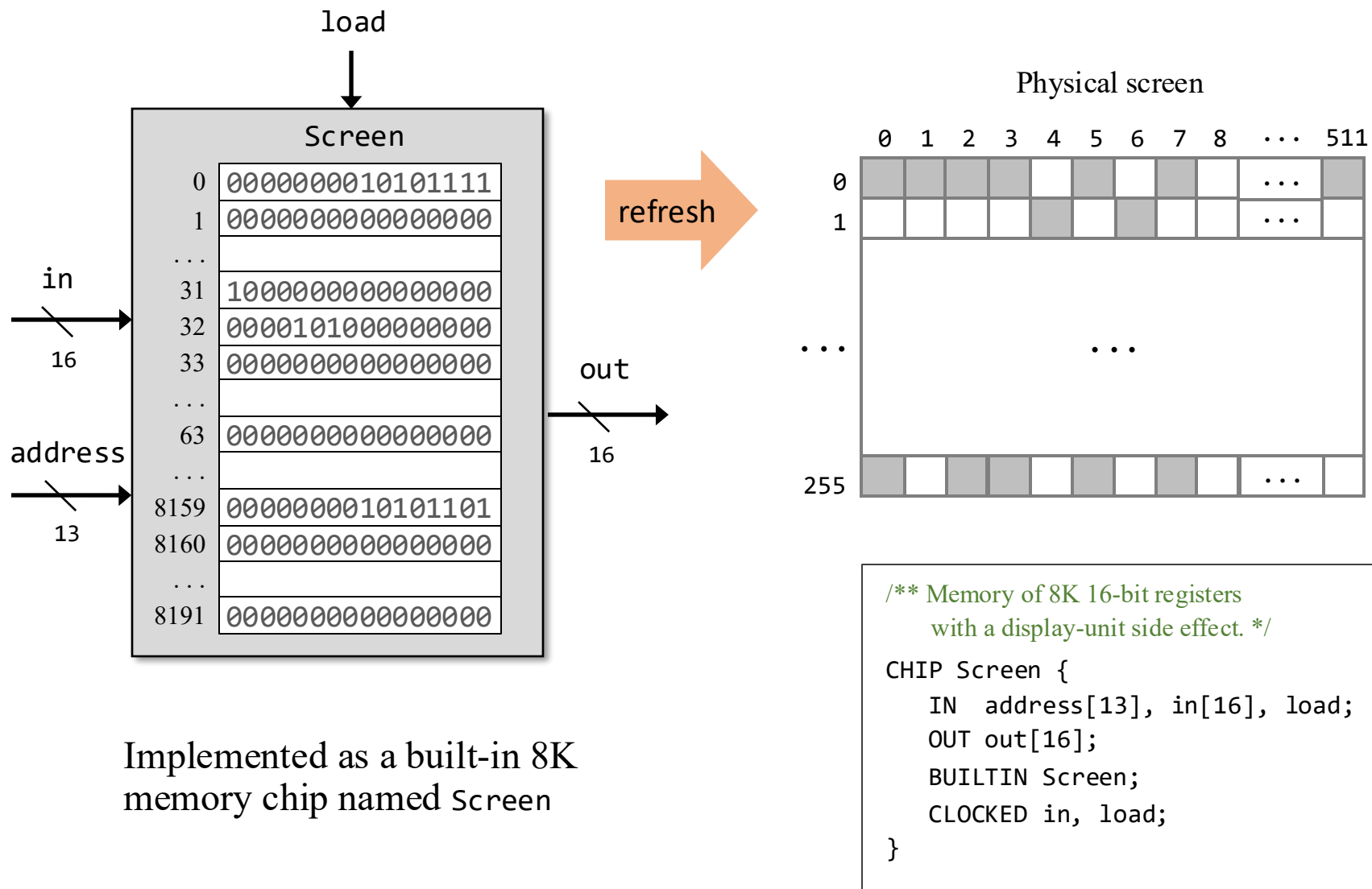


# Keyboard

 

# Keyboard

 

# Keyboard

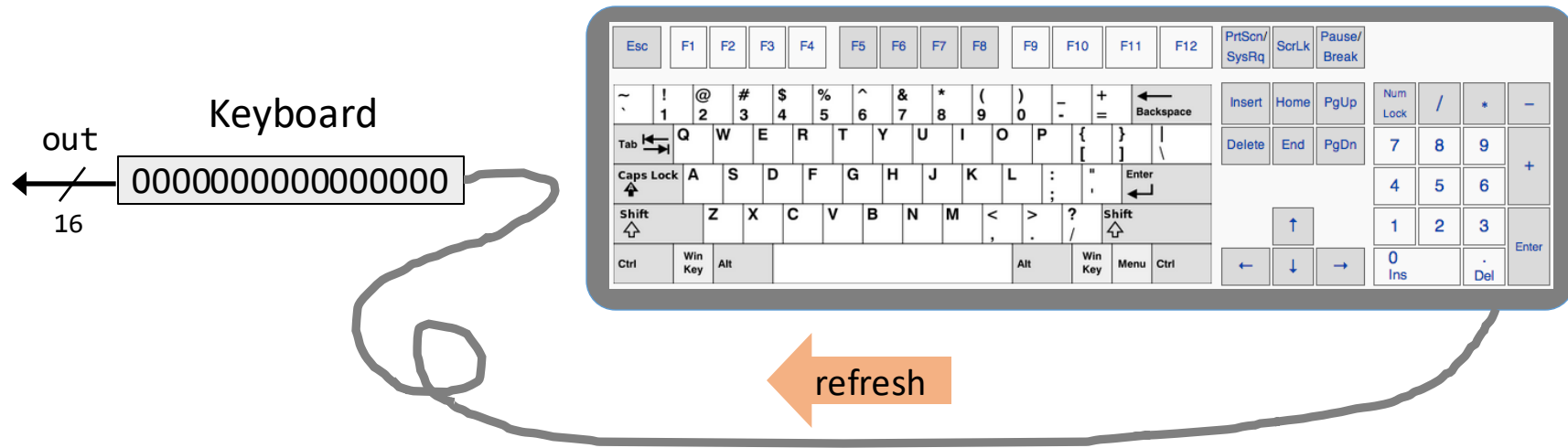

Implemented as a built-in  
16-bit memory register  
named Keyboard

```
/** 16-bit register, outputs the character code of the currently  
    pressed keyboard key, or 0 if no key is pressed */  
CHIP Keyboard {  
    OUT  
    out[16];  
    BUILTIN Keyboard;  
}
```



# Chapter 5: Computer Architecture

---

✓ Basic architecture

✓ Fetch-Execute cycle

✓ The Hack CPU


✓ Input / output



Memory


- Computer
- Project 5: Chips
- Project 5: Guidelines

# Memory

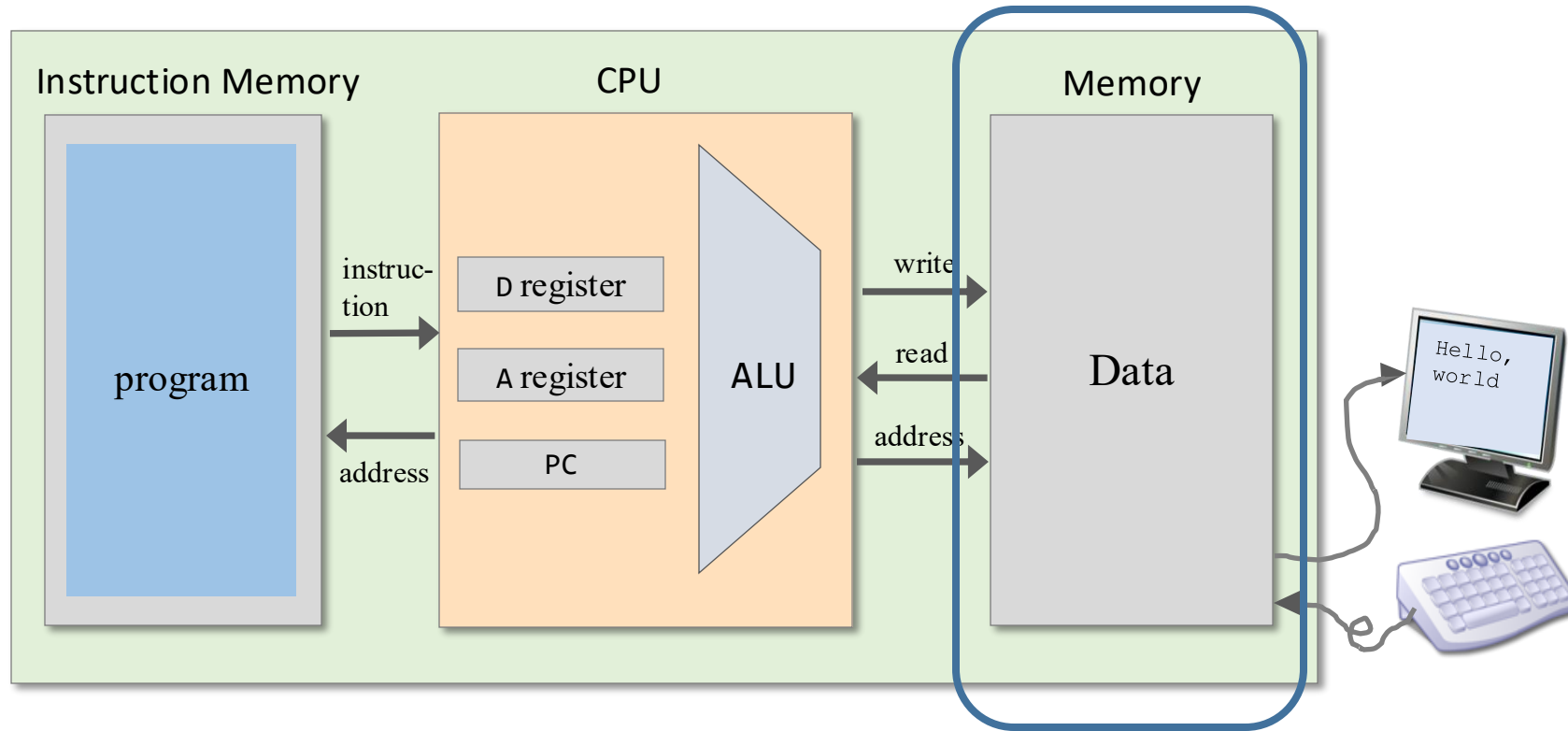


# Memory: Implementation

---

 


# Memory: Implementation

---

 


# Memory: Implementation

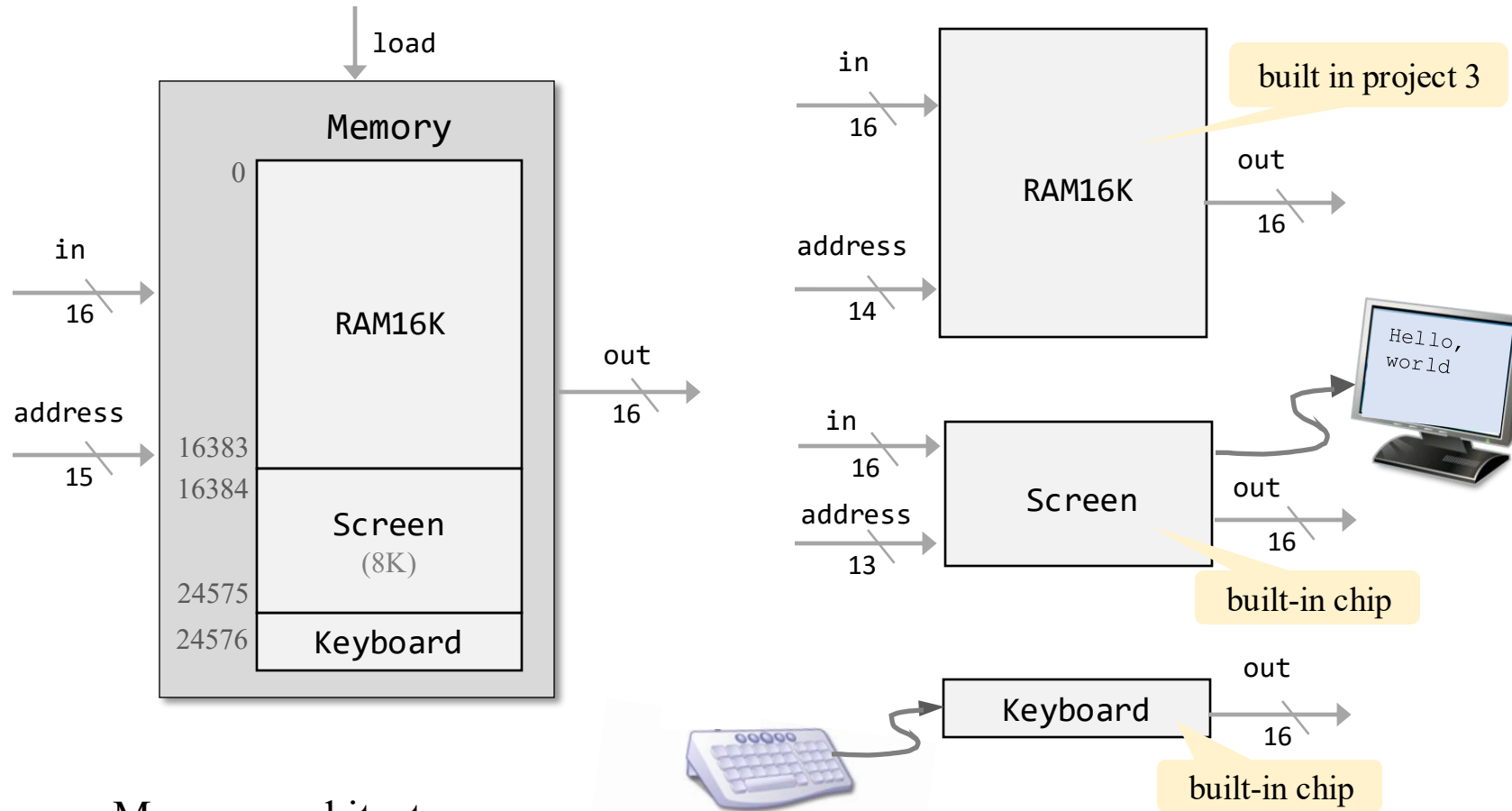


## Memory architecture

- An aggregate of three chip-parts: RAM16K, Screen, Keyboard
- Single address space, 0 to 24576 (0x6000)
- Maps the address input onto the address input of the relevant chip-part.

# Instruction memory

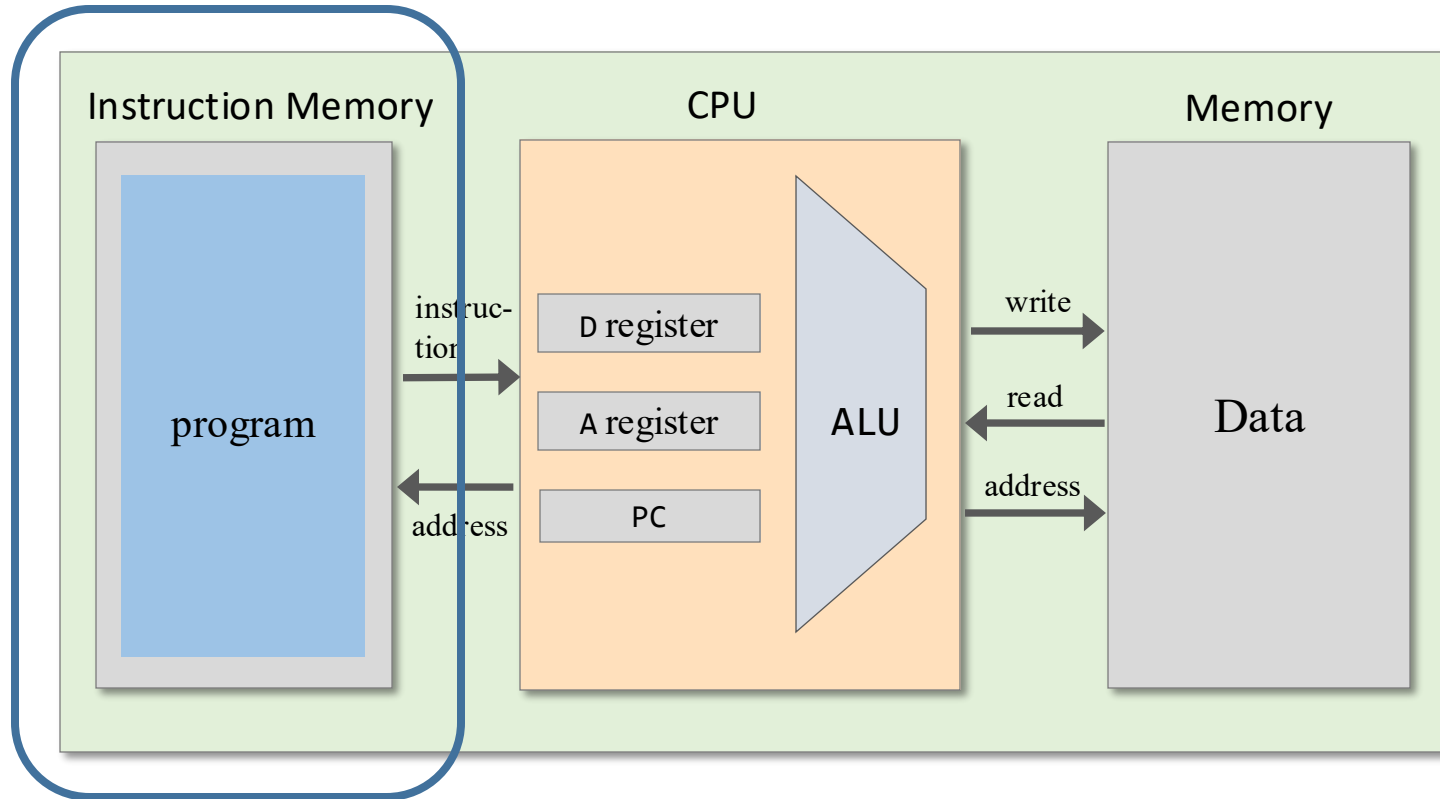

# Instruction memory

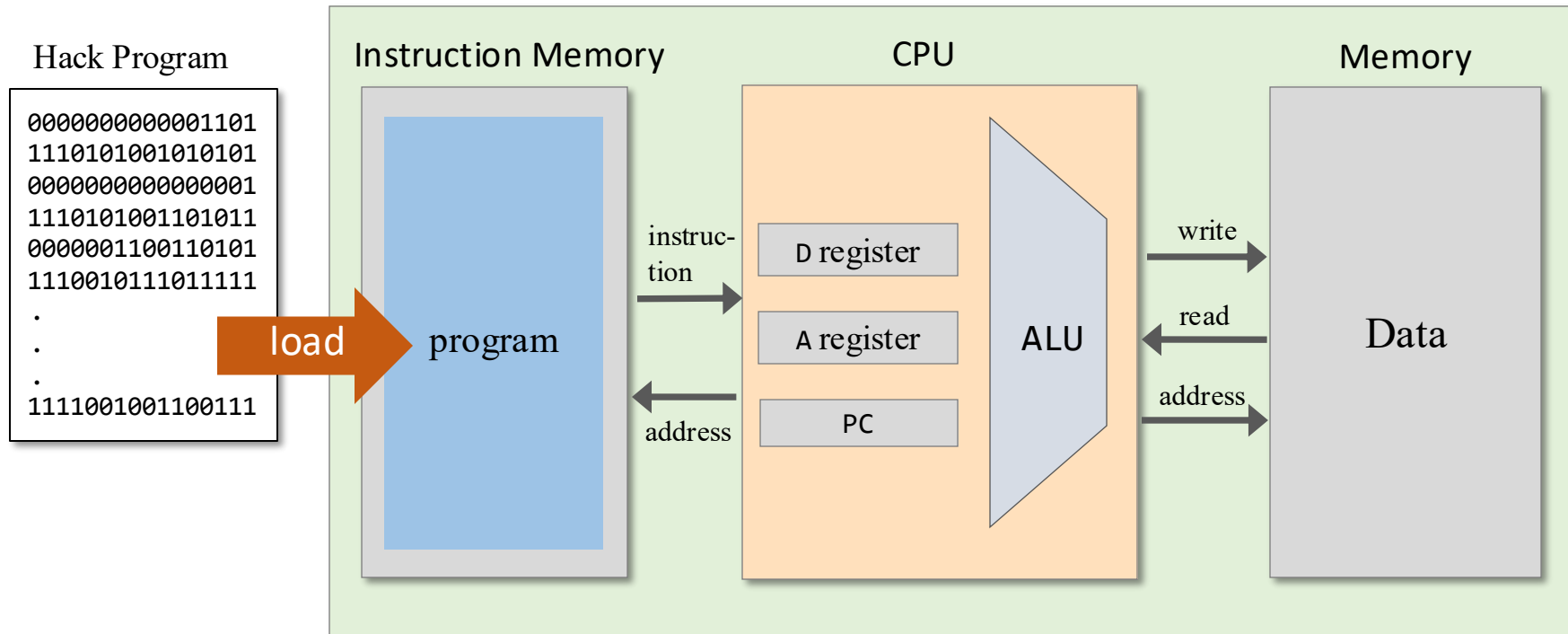


## Instruction memory

Implemented as a built-in plug-and-play chip named ROM32K  
(pre-loaded with a program)

## Loading a program

- Physical: Replace the ROM chip
- Simulator: Load a file containing instructions

# Instruction memory

 

## Instruction memory

Implemented as a built-in plug-and-play chip named ROM32K  
(pre-loaded with a program)

```
/** Read-Only memory (ROM),  
    acts as the Hack computer instruction memory. */  
CHIP ROM32K {  
    IN  address[15];  
    OUT out[16];  
    BUILTIN ROM32K;  
}
```



# Chapter 5: Computer Architecture

---

- Basic architecture

✓ Memory

- Fetch-Execute cycle

➔ Computer

- The Hack CPU


- Project 5: Chips

- Input / output

- Project 5: Guidelines

# Hack computer architecture

---

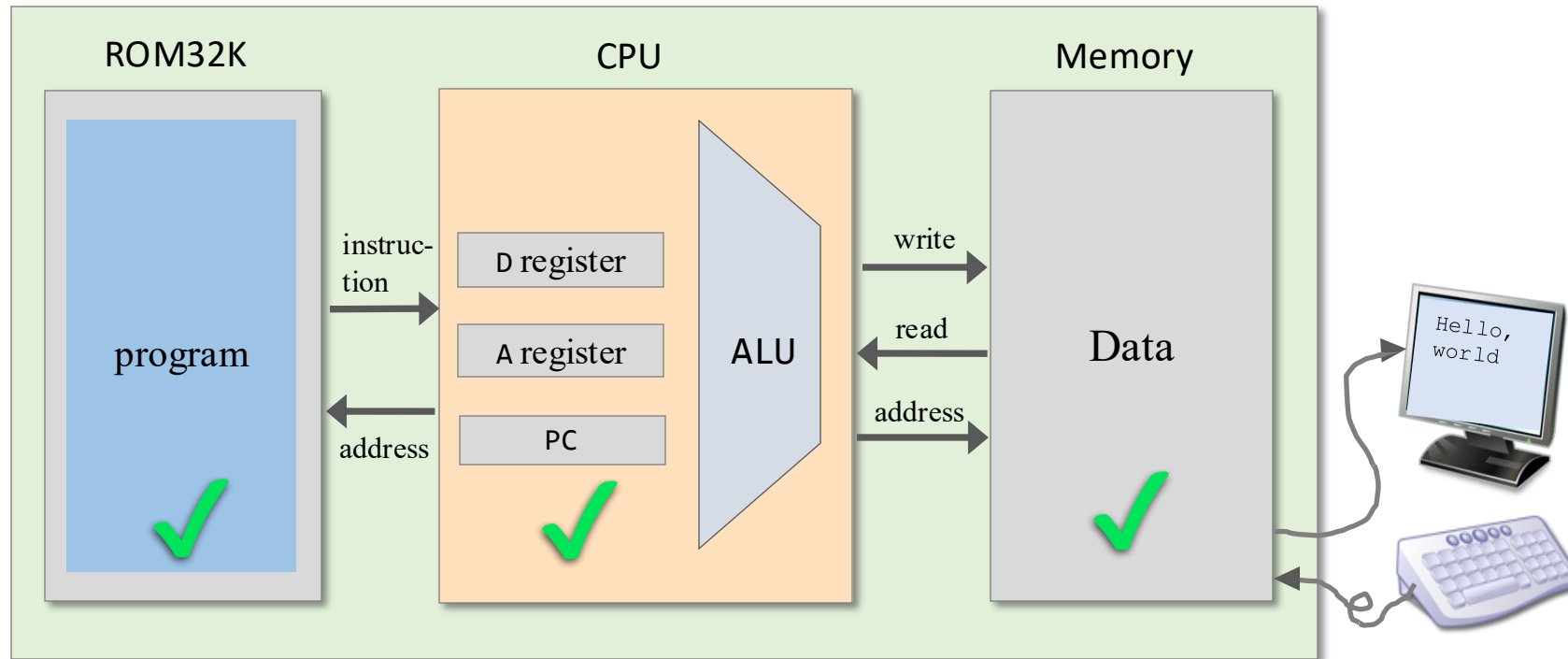


## Remaining challenge

Integrate into a single chip, named Computer

# Computer abstraction

---

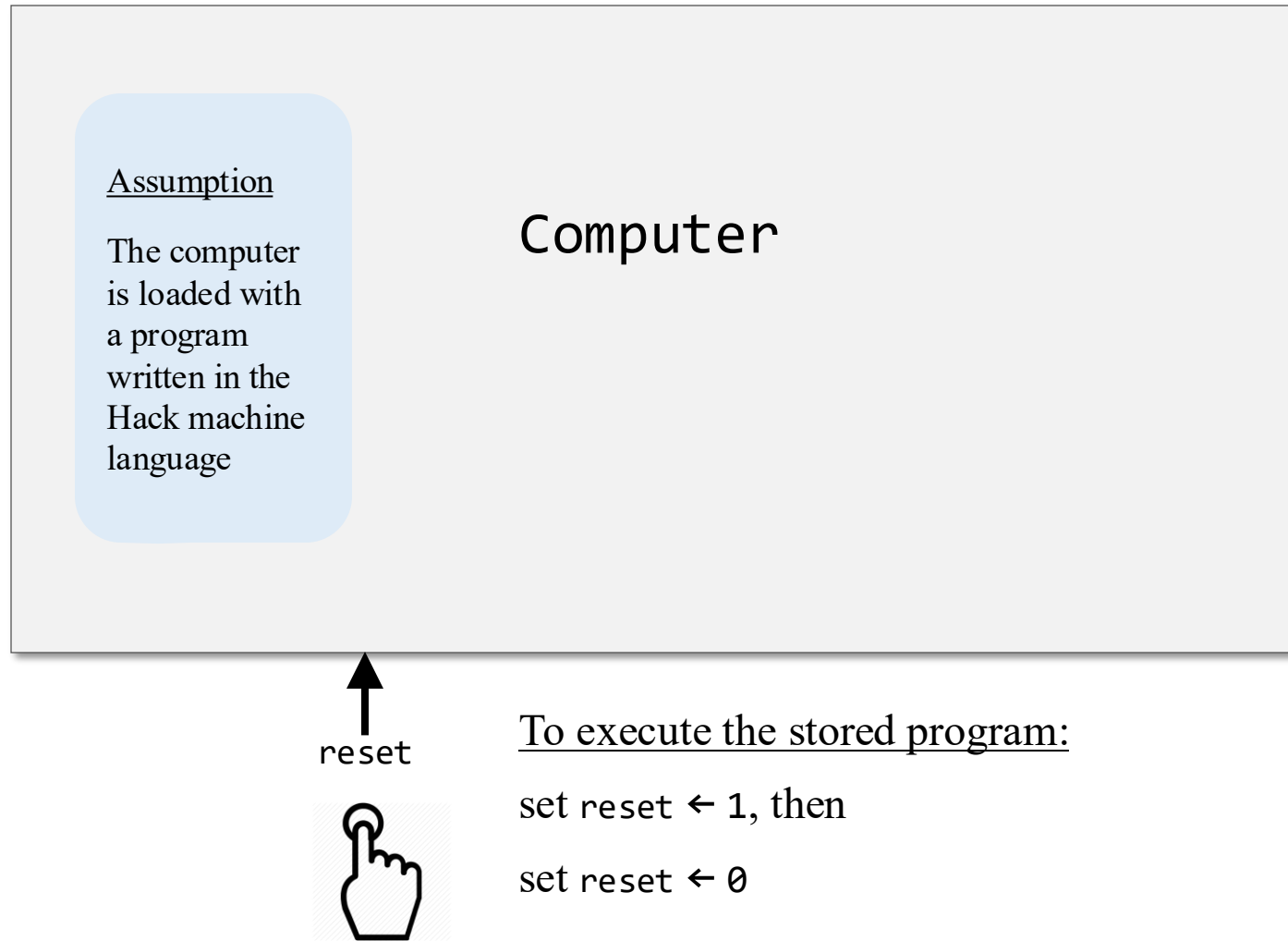

# Computer abstraction

---

## Assumption

The computer is loaded with a program written in the Hack machine language

## Computer

if ( $\text{reset} == 1$ ), executes the *first* instruction in the stored program

if ( $\text{reset} == 0$ ), executes the *next* instruction in the stored program

↑  
reset




## To execute the stored program:

set  $\text{reset} \leftarrow 1$ , then


set  $\text{reset} \leftarrow 0$

# Computer implementation

---

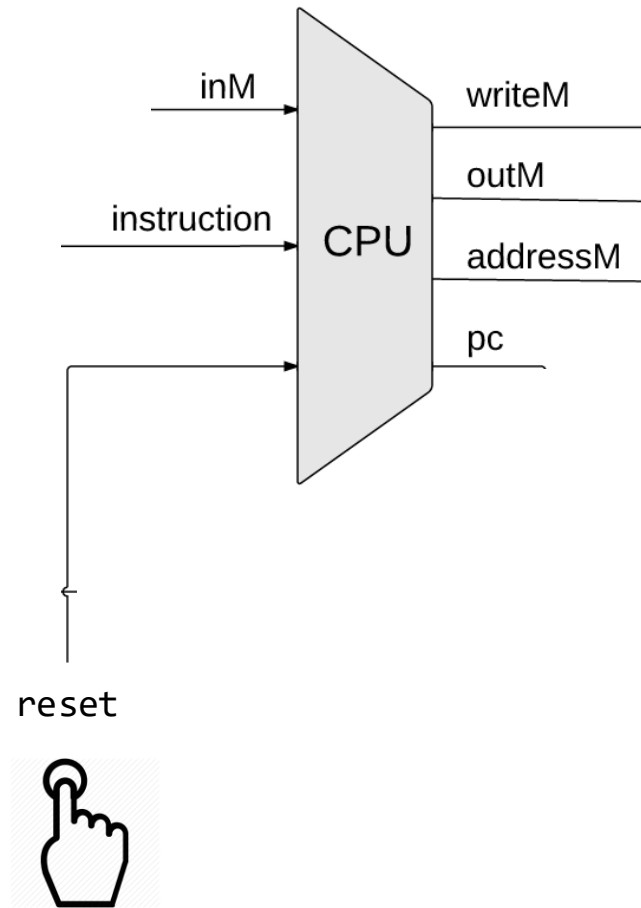

# Computer implementation

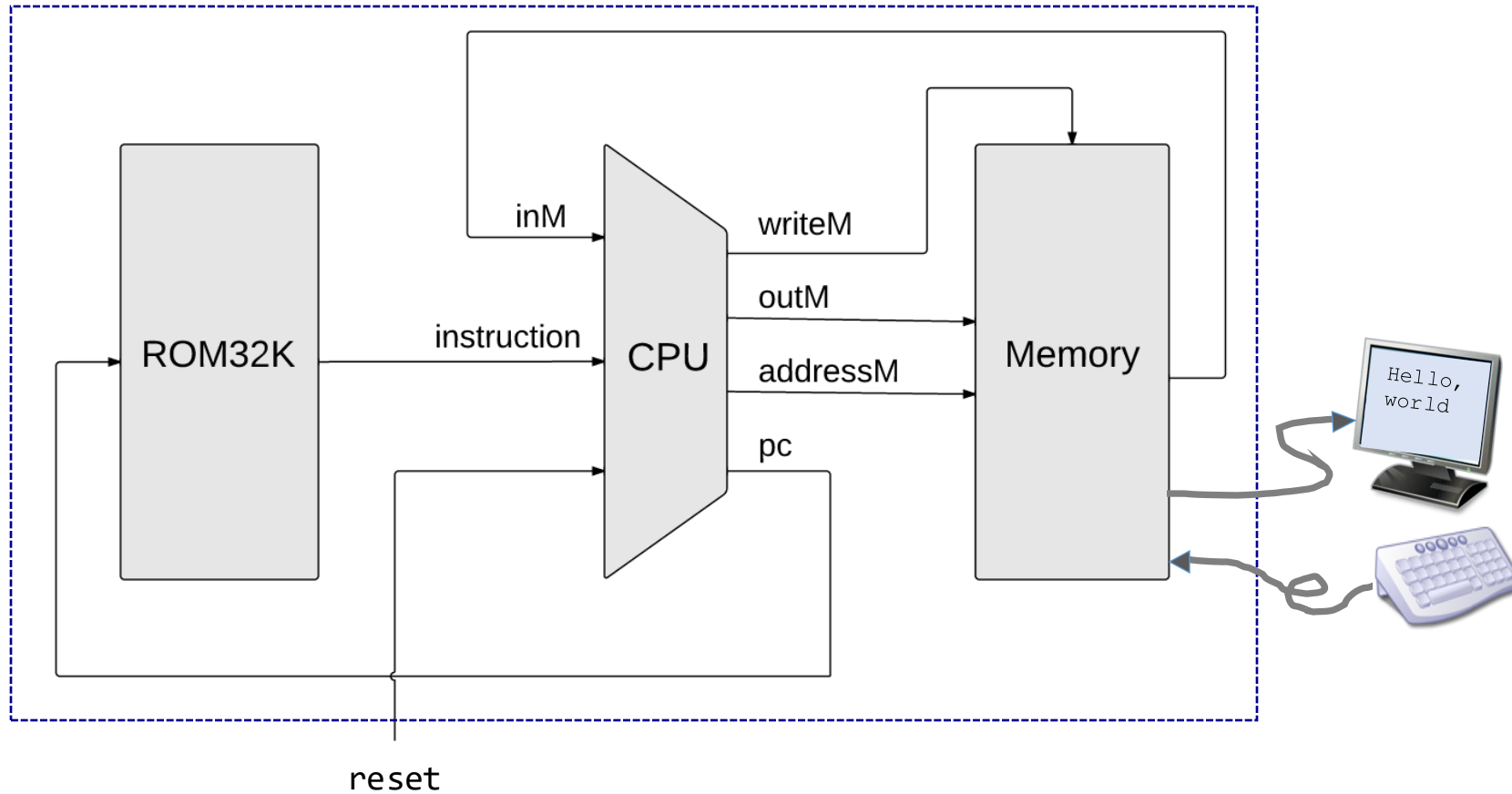


reset



## Implementation

Connect the three chip-parts  
along these lines.

# Computer implementation

 

# Computer Architecture


---

- Basic architecture
  - Fetch-Execute cycle
  - The Hack CPU
  - Input / output
- ✓ Memory
  - ✓ Computer
  - ➔ Project 5: Chips
    - Project 5: Guidelines



# Computer Architecture

---

 

## Project 5




- CPU
- Memory
- Computer

# CPU


```
/** Central Processing unit.
    Executes instructions written in Hack machine language.
CHIP CPU {
    IN
        inM[16],          // Value of M (RAM[A])
        instruction[16],  // Instruction to execute
        reset;             // Signals whether to execute the first instruction
                           // (reset==1) or next instruction (reset == 0)

    OUT
        outM[16]          // Value to write to the selected RAM register
        writeM,           // Write to the RAM?
        addressM[15],     // Address of the selected RAM register
        pc[15];           // Address of the next instruction

     PARTS:
        //// Put you code here
}
```




# CPU

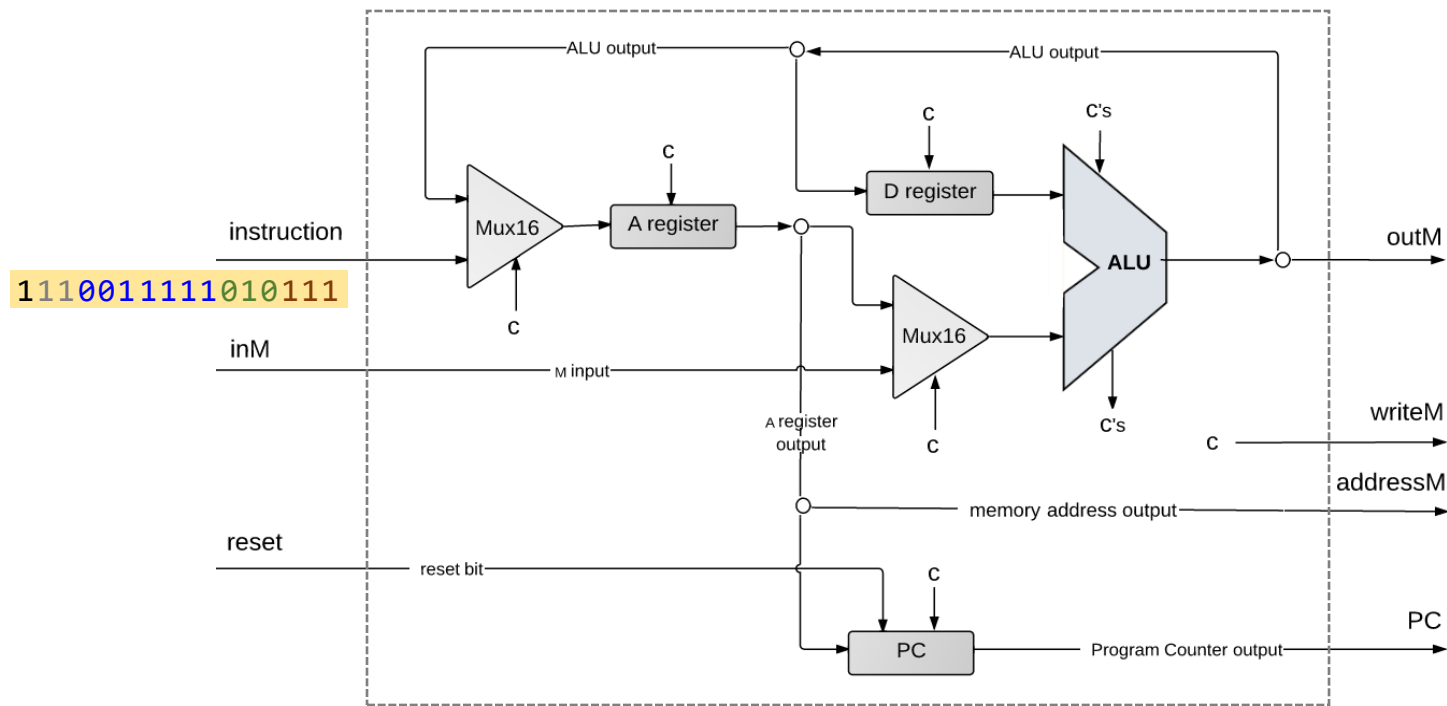

## Implementation tips

- All the chip-parts seen here were built in projects 1, 2, 3
- But: we'll use their built-in versions
- Use HDL to unpack the instruction bits and connect them to the control bits of chip-parts
- Use gate logic to compute the address of the next instruction.

# Computer Architecture

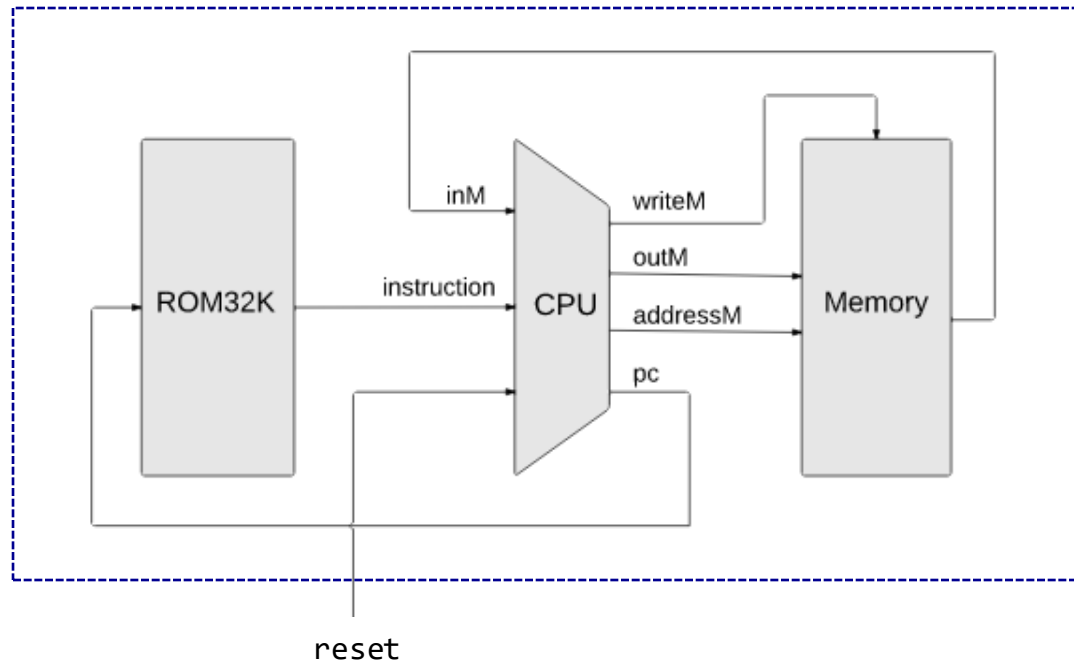


## Project 5:

✓ CPU

➔ Memory

- Computer

# Memory

 

## Memory.hdl

```
/** Complete address space of the computer's data memory,
    including RAM, screen memory map, and keyboard memory map.
    Outputs the value of the memory location specified by address.
    If (load==1), the in value is loaded into the memory location specified by address.

    Addressing space rules:
    Only the upper 16K+8K+1 words of the memory are used.


    Access to address 0 to 16383 (0x0000 to 0x3FFF) results in accessing the RAM;
    Access to address 16384 to 24575 (0x4000 to 0x5FFF) results in accessing the Screen memory map;
    Access to address 24576 (0x6000) results in accessing the Keyboard memory map.
*/

CHIP Memory {
    IN    address[15], in[16], load;
    OUT   out[16];
    PARTS:
        //// Put your code here.
}
```

## Implementation tips

- Two bits in the address input can be used to determine the target memory-part (RAM16K, Screen, Keyboard)
- The remaining bits of the address input are the target address within the target memory-part
- Do the read/write specified by the Memory's inputs, and output the value of the selected memory-part[address] to the Memory's out output.

# Memory

 

## Memory.hdl

```
/** Complete address space of the computer's data memory,
    including RAM, screen memory map, and keyboard memory map.
    Outputs the value of the memory location specified by address.
    If (load==1), the in value is loaded into the memory location specified by address.

    Addressing space rules:
    Only the upper 16K+8K+1 words of the memory are used.

    Access to address 0 to 16383 (0x0000 to 0x3FFF) results in accessing the RAM;
    Access to address 16384 to 24575 (0x4000 to 0x5FFF) results in accessing the Screen memory map;
    Access to address 24576 (0x6000) results in accessing the Keyboard memory map.
*/

CHIP Memory {
    IN    address[15], in[16], load;
    OUT   out[16];
    PARTS:
        //// Put your code here.
}
```


## Implementation tips (continued)

- Use builtin memory-parts (RAM16K, Screen, Keyboard), and builtin logic gates, as needed.
- Optional: Start by building a basic Memory chip that outputs two bits, say, loadRAM and loadScreen, indicating if the addressed memory-part is the RAM or the Screen

Then complete the final Memory chip, in which these two bits can become internal pins.

# Computer

---

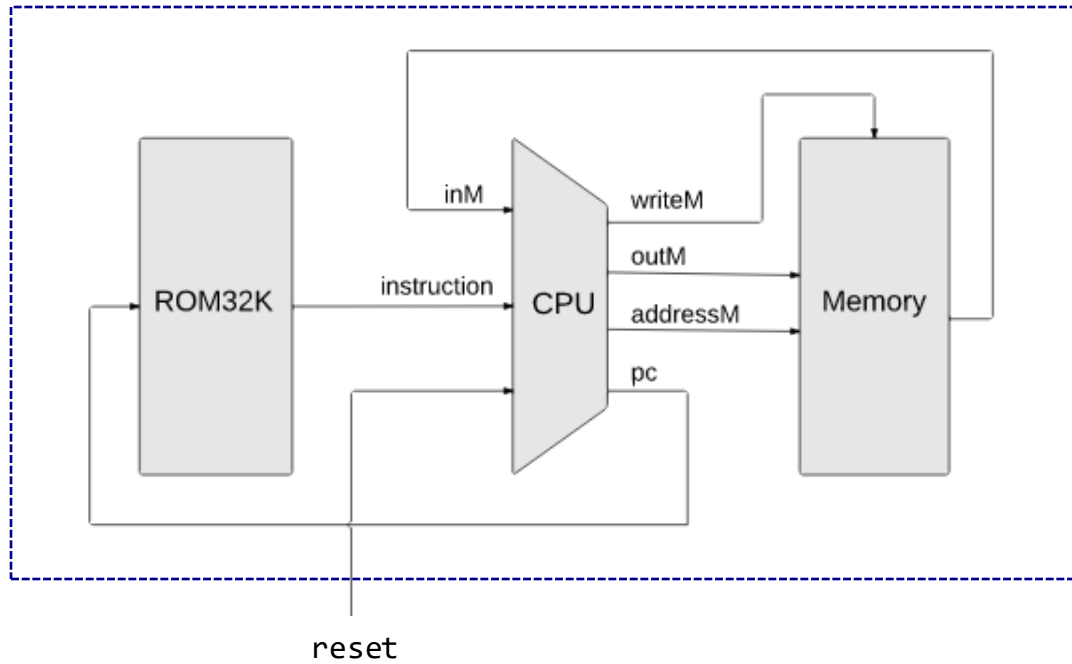


## Project 5:

✓ CPU

✓ Memory

➡ Computer

# Computer

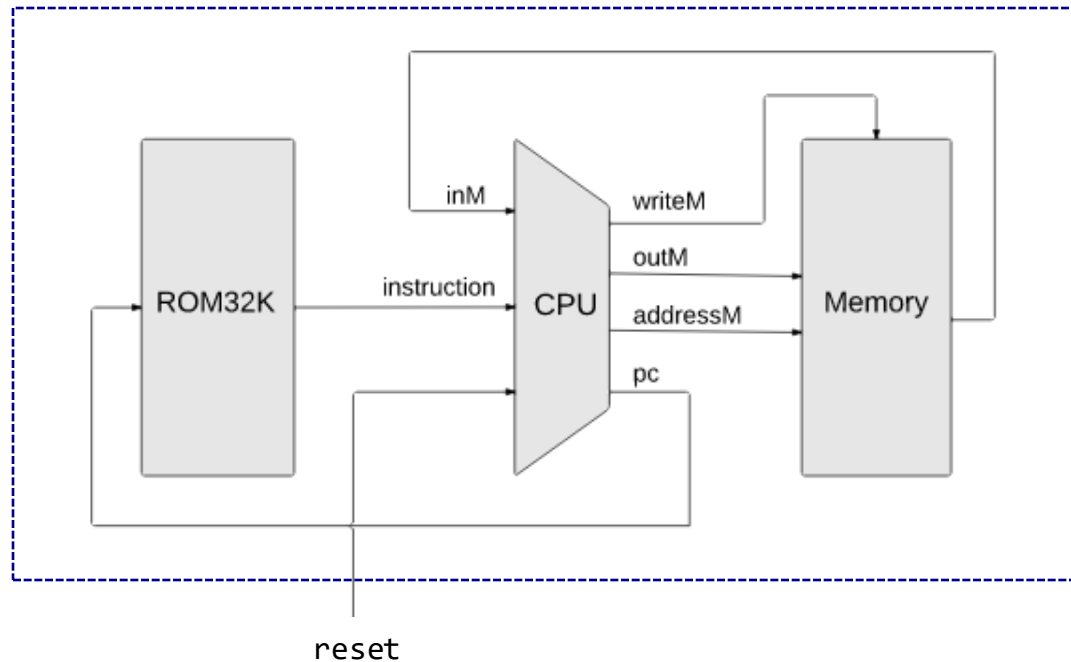

```
/** The Hack computer, including CPU, RAM and ROM, loaded with a program.  
    When (reset==1), the computer executes the first instruction in the program;  
    When (reset==0), the computer executes the next instruction in the program. */
```

```
CHIP Computer {  
    IN reset;  
    PARTS:  
        // Put your code here.  
}
```

## Implementation tips

Use the built-in ROM32K

Follow the diagram, and use HDL to connect the three chip-parts



# Computer Architecture

---

- Basic architecture
  - Fetch-Execute cycle
  - The Hack CPU
  - Input / output
- ✓ Memory
  - ✓ Computer
  - ✓ Project 5: Chips
  - ➔ Project 5: Testing

# Testing the Computer chip

---

## Testing logic

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

Computer.hdl

```
/** The Hack computer, including CPU, RAM and ROM,  
    loaded with a program. */  
CHIP Computer {  
    IN reset;  
    PARTS:  
    //// Completed HDL code  
}
```

# Testing the Computer chip

---

## Testing logic

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

Computer.hdl

```
/** The Hack computer, including CPU, RAM and ROM,  
    loaded with a program. */  
CHIP Computer {  
    IN reset;  
    PARTS:  
    //// Completed HDL code  
}
```

## Test programs


- Add.hack:  
RAM[0]  $\leftarrow 2 + 3$
- Max.hack:  
RAM[2]  $\leftarrow \max(\text{RAM}[0], \text{RAM}[1])$
- Rect.hack:  
Draws a rectangle of RAM[0] rows  
of 16 pixels each.

# Testing the Computer chip

## Testing logic

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs

- Add.hack:  
RAM[0]  $\leftarrow 2 + 3$
-  Max.hack:  
RAM[2]  $\leftarrow \max(\text{RAM}[0], \text{RAM}[1])$
- Rect.hack:  
Draws a rectangle of RAM[0] rows of 16 pixels each.

ComputerMax.tst


```
load Computer.hdl,  
output-file ComputerMax.out,  
compare-to ComputerMax.cmp,  
output-list time reset ARegister[] DRegister[] PC[]  
          RAM16K[0] RAM16K[1] RAM16K[2];  
  
// Loads a Hack program (that computes R2 = max(R0,R1))  
ROM32K load Max.hack,
```

# Testing the Computer chip

## Testing logic

- Load Computer.hdl into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs

- Add.hack:  
RAM[0]  $\leftarrow 2 + 3$
-  Max.hack:  
RAM[2]  $\leftarrow \max(\text{RAM}[0], \text{RAM}[1])$
- Rect.hack:  
Draws a rectangle of RAM[0] rows of 16 pixels each.

### ComputerMax.tst

```
load Computer.hdl,
output-file ComputerMax.out,
compare-to ComputerMax.cmp,
output-list time reset ARegister[] DRegister[] PC[]
          RAM16K[0] RAM16K[1] RAM16K[2];

// Loads a Hack program (that computes R2 = max(R0,R1))
ROM32K load Max.hack,

// Test 1: computes max(3,5)
set RAM16K[0] 3,
set RAM16K[1] 5,
output;
repeat 14 {
    tick, tock, output;
}

// Resets the PC
set reset 1,
tick, tock, output;

// Test 2: computes max(23456,12345)
set reset 0,
set RAM16K[0] 23456,
set RAM16K[1] 12345,
output;
repeat 14 {
    tick, tock, output;
}
```

# Testing the Computer chip

---

## Testing logic

- Load `Computer.hdl` into the hardware simulator
- Load a Hack program into the ROM32K chip-part
- Run the clock enough cycles to execute the program

## Test programs


- `Add.hack`:  
 $\text{RAM}[0] \leftarrow 2 + 3$
- `Max.hack`:  
 $\text{RAM}[2] \leftarrow \max(\text{RAM}[0], \text{RAM}[1])$



`Rect.hack`:

Draws a rectangle of  $\text{RAM}[0]$  rows of 16 pixels each.


`Rect.hack` output:

 

## Test script

- `ComputerRect.tst`
- Inspect it, understand the testing logic.

# What's next?

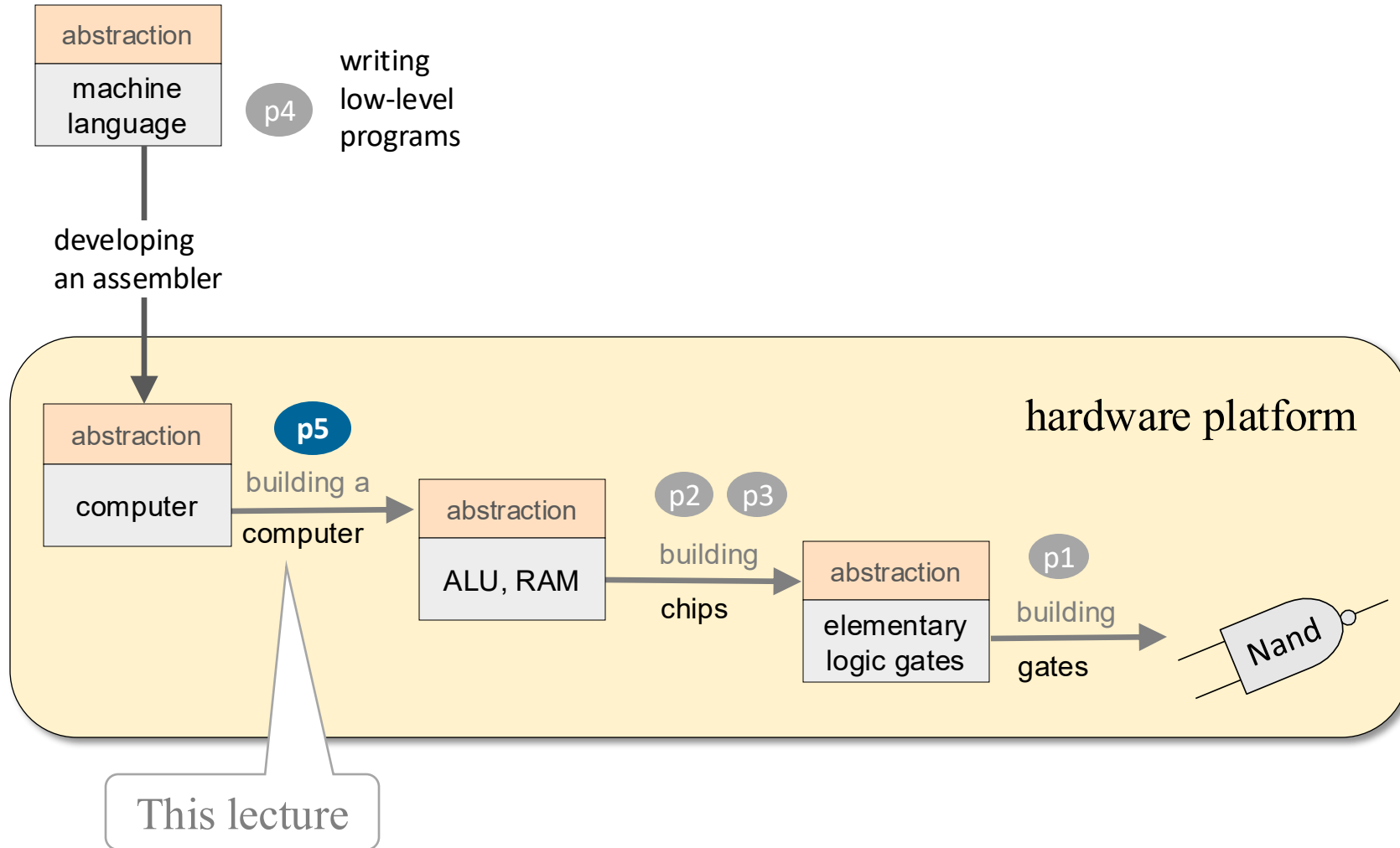

# What's next?

